



HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY
COMPUTER ENGINEERING

Electronic Device Component



Dr. Le Trong Nhan

Contents

Chapter 1. Bipolar Junction Transistor	7
1 Introduction	8
2 BJT simulation circuit	9
3 Exercise and Report	10
3.1 BJT in Saturation Mode	10
3.2 DC Sweep Simulation	11
3.3 BJT used as a Switch	12
3.4 Drive a device with an NPN BJT	14
3.4.1 Theory calculations	14
3.4.2 Simulation	15
3.4.3 Compare	16
3.5 Simple bias configuration	17
3.5.1 Simulation	17
3.5.2 Circuit analysis	19
3.6 PNP Circuit	21
3.6.1 Theoretical calculation	21
3.6.2 Simulation	22
3.6.3 Comparison	22
3.7 Circuit with NPN and PNP bipolar junction transistors	23
3.7.1 Theoretical calculation	23
3.7.2 Simulation	24
3.7.3 Comparison	24

CHAPTER 1

Bipolar Junction Transistor

1 Introduction

In the diode tutorials we saw that simple diodes are made up from two pieces of semiconductor material to form a simple pn-junction and we also learnt about their properties and characteristics.

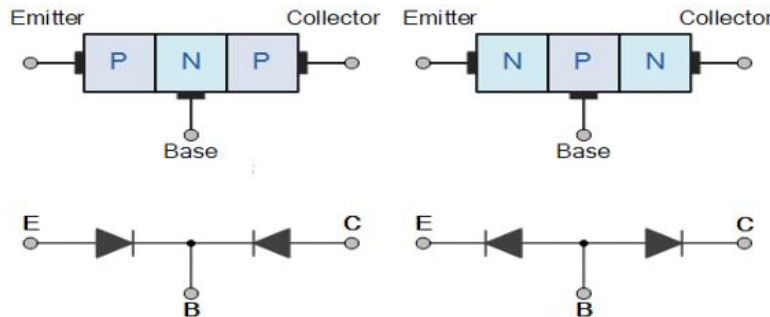


Figure 1.1: Bipolar transistor construction

If two individual signal diodes are joined together back-to-back, this will form a two PN-junctions connected together in series which would share a common Positive, (P) or Negative, (N) terminal. The fusion of these two diodes produces a three layer, two junction, three terminal device forming the basis of a Bipolar Junction Transistor (BJT), which is shown in the figure above.

Considering the symbol of the transistor in the schematic, the direction of the arrow always points from the positive P-type region to the negative N-type region for both transistor types, exactly the same as for the standard diode symbol.

The transistor is ability to change between these two states enables it to have two basic functions: “switching” (digital electronics) or “amplification” (analogue electronics). Then bipolar transistors have the ability to operate within three different regions:

- Active region: The transistor operates as an amplifier and $I_C = \beta I_B$
- Saturation: The transistor is “Fully-ON” operating as a switch and $I_C = I_{Sat}$
- Cut-off: The transistor is “Fully-OFF” operating as a switch and $I_C = 0$

2 BJT simulation circuit

Implement the following circuit in PSPICE. The new component used is **QBreakN NPN**, which can be found in the Favorites list. The default transistor gain is $\beta = 100$, and the saturated voltage $V_{CE(Sat)} = 0.65V$

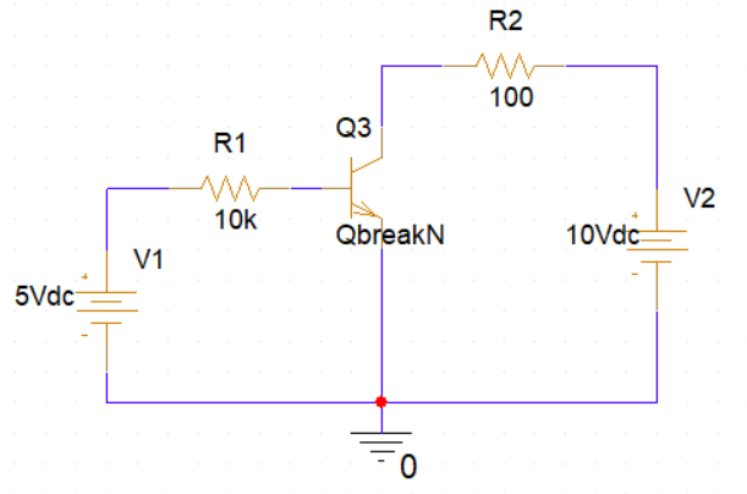


Figure 1.2: Simple connection with transistor

For a bias point simulation profile, the following results are expected:

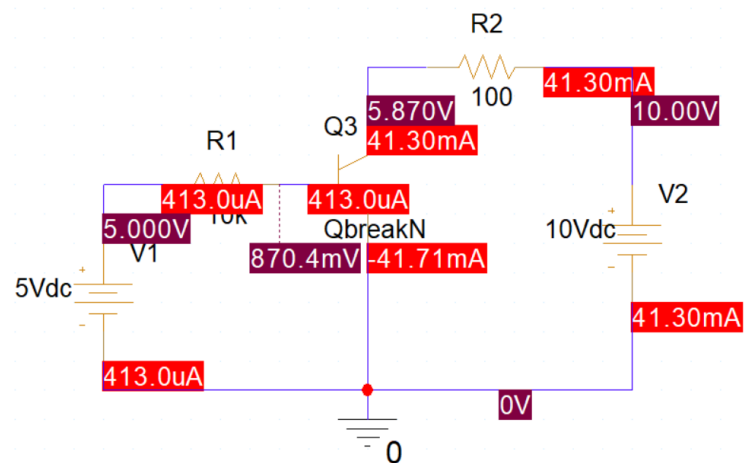


Figure 1.3: Bias profile simulation results

It is assumed that $V_{BE} = 0.7V$, the simulation results in PSpice are explained as follows:

- According to the Ohm Law, $I_B = (V_{BB} - V_{BE}) / R1 = (5V - 0.7V) / 10k = 0.43mA$
- It is assumed that the transistor is in linear (or active) mode, $I_C = \beta * I_B = 43mA$
- Finally, in order to confirm the assumption above, $V_{CE} = V_{CC} - I_C * R2 = 10V - 43mA * 100\Omega = 5.7V$


Since $V_{CE} > V_{CE(Sat)}$, the transistor is working in the linear mode, to confirm our assumption. Moreover, the theory calculation is very close to the PSpice simulations.

3 Exercise and Report

3.1 BJT in Saturation Mode

Change the value of **R1 to 1k** and run the simulation again. Capture the simulation results and explain the values of I_B , I_C , V_{CE} . The default transistor gain is $\beta = 100$, and the saturated voltage $V_{CE(Sat)} = 0.65V$ and $V_{BE} = 0.7V$.

Your image goes here:

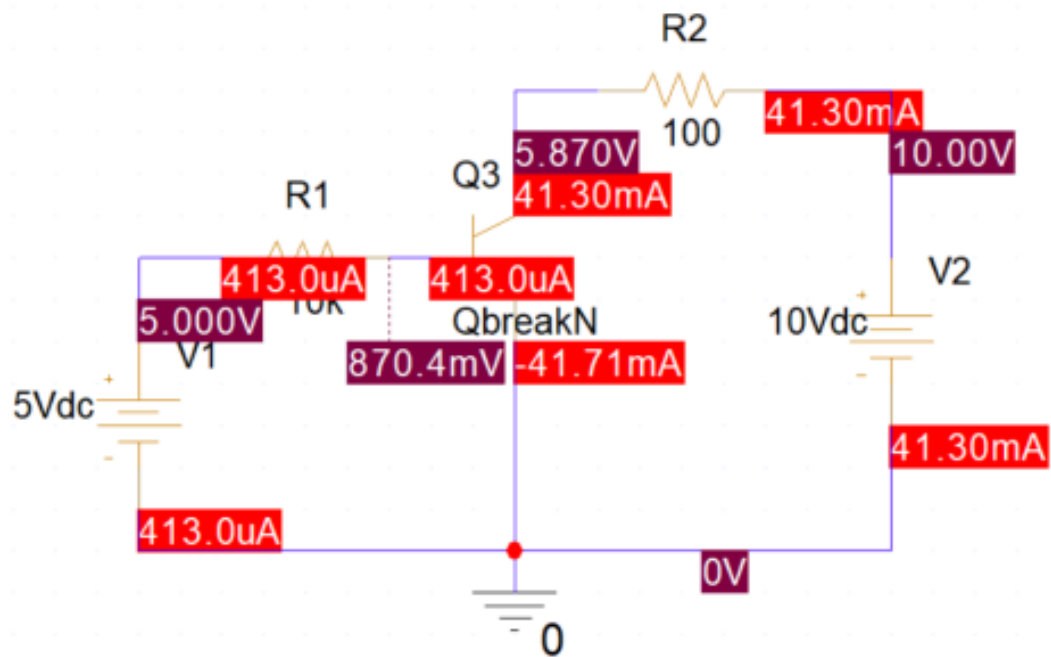

The results in PSpice are explained as follows:

According to the Ohm Law:

$$I_B = \frac{V_1 - V_{BE}}{R_1} = \frac{5V - 0.7V}{1k} = 4.3 \text{ (mA)}$$

Let the transistor be in linear (or active) mode: $I_C = \beta \cdot I_B = 0.43 \text{ (A)}$

Testing: $V_{CE} = V_2 - I_C \cdot R_2 = 10V - 0.43 \cdot 100 = -33 \text{ (V)}$

Because $V_{CE} < 0$, the transistor is saturated. We have now:

$$I_C = \frac{V_2 - V_{CE(Sat)}}{R_2} = \frac{10 - 0.65}{100} = 93.5 \text{ (A)}$$

3.2 DC Sweep Simulation

The schematic in the first exercise with $R1 = 1k$ is re-used in this exercise. However, a DC-Sweep simulation mode is performed with V1 is varied from 0V to 5V (0.1V for the step), as follows:


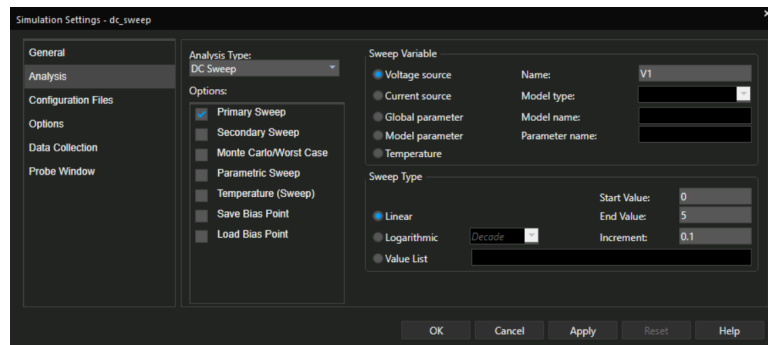


Figure 1.4: DC-Sweep profile for simulation

Run the simulation and trace for the current I_C according to the value of V1. Capture your screen and plot it in the report. Please increase the width of the curve.

Your image goes here:

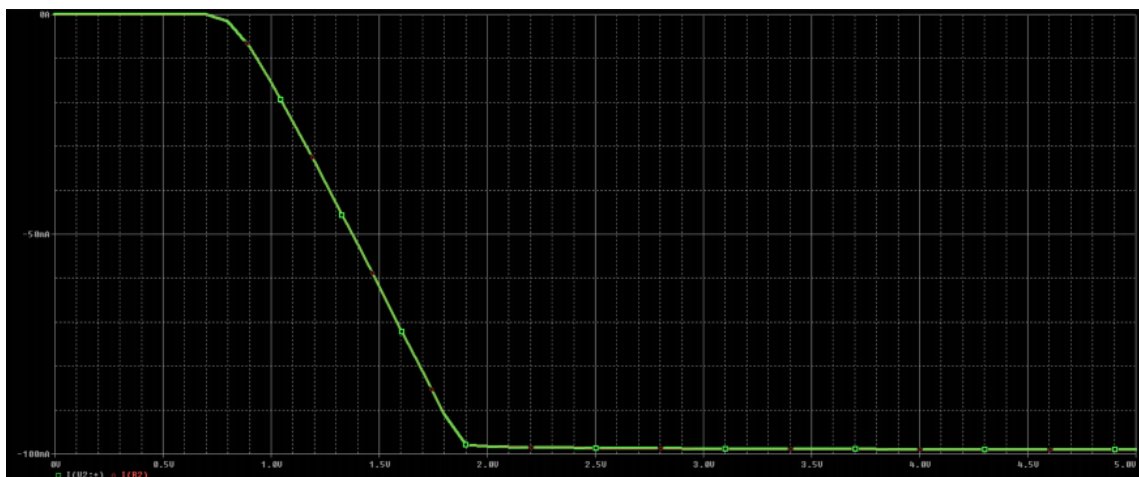

When the transistor becomes saturation, the value of V1 is 1.9 V.

$$\text{Meanwhile: } I_B = \frac{I_C}{\beta} = \frac{97.889}{100} = 0.98 \text{ (mA)}$$

$I_{C(saturated)}$ is 97.89 (mA)

3.3 BJT used as a Switch

For a given BJT circuit, determine R1 and R2 to have IC saturated at 50mA. In this saturation mode, $V_{CE(Sat)}$ is 30mV. Assume that $V_{BE} = 0.7V$ and the current gain $\beta = 100$.

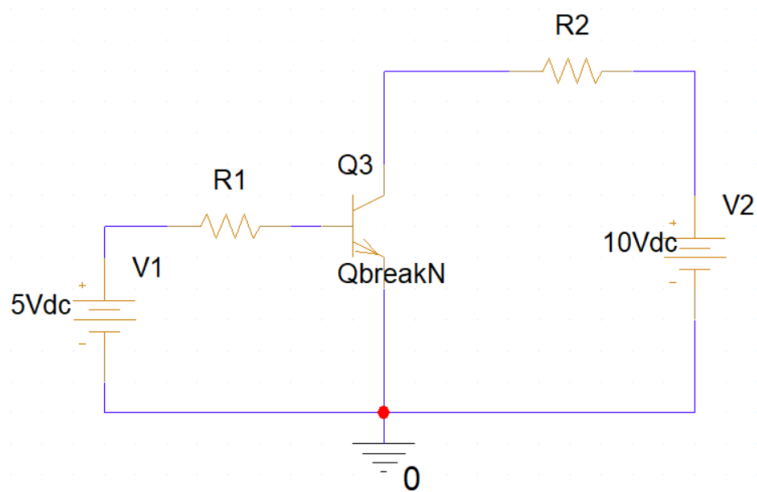


Figure 1.5: BJT used as switch in saturation mode

Present your solution to determine R1 and R2. Perform the simulation in PSpice to confirm the results. Capture the screen in PSpice and present in the report.


$$I_C \text{ saturated at } 50 \text{ mA} \Rightarrow I_C = 50 \text{ (mA)}$$

$$I_C \leq \beta \cdot I_B \Rightarrow I_B \geq 0.5 \text{ (mA)}$$

$$I_B = \frac{V_1 - 0.7}{R_1} = \frac{5 - 0.7}{R_1} \geq 0.5 \Rightarrow R_1 \leq 8.6k \text{ (Ohm)}$$

$$I_C = \frac{V_2 - V_{CE}}{R_2} = \frac{10 - 0.03}{R_2} = 50 \Rightarrow R_2 \geq 199.4 \text{ (Ohm)}$$

Your image goes here:

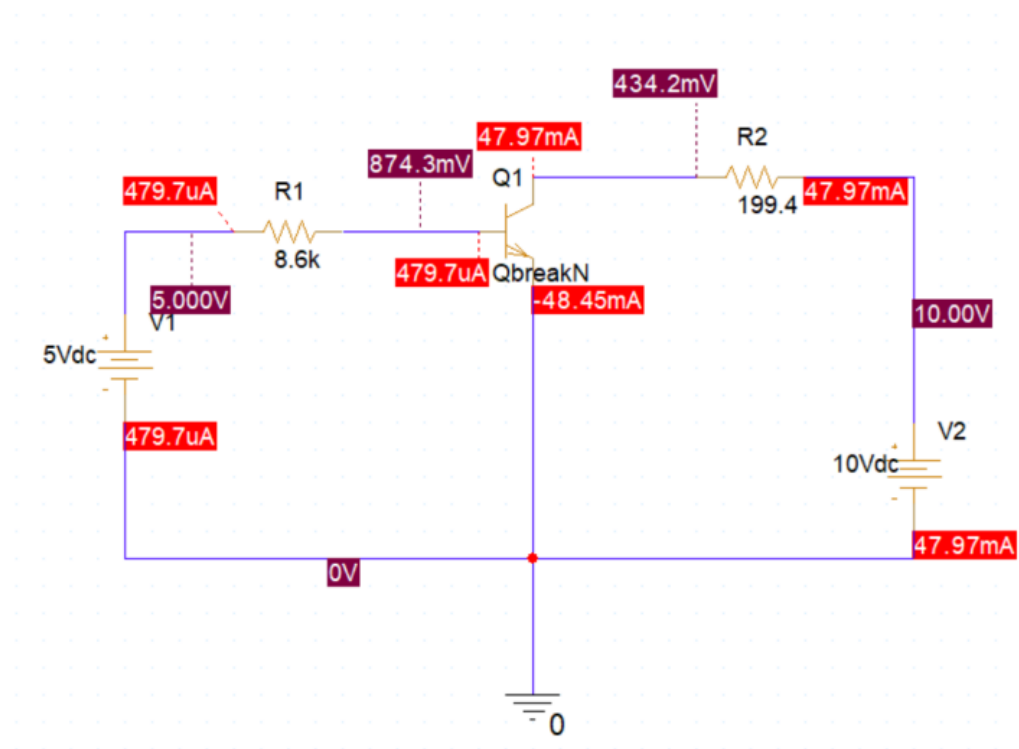

3.4 Drive a device with an NPN BJT

This exercise has a 5V logic output (the V_{ter} in Figure 1.6) that can source up to 10mA of current without a severe voltage drop and stand a maximum current of 20mA. If the logic terminal sources a current larger than 20mA, it would be damaged. Or, if it sources a current larger than 10mA, the V_{ter} voltage will drop to less than 4V. We should avoid this drop in many cases. However, this logic terminal has to be used to drive an electrical component with an equivalent internal resistance of 5 ohms (the LOAD in Figure 1.6) and requires a current of at least 300mA and not exceeding 500mA to function normally. Given that we have an NPN transistor with the current gain β equals 100, the maximum I_C current is 400mA, and the barrier potential at the BE junction is $V_{BE} = 0.7V$, select a resistor available in the market to replace the resistor R_B revealed in Figure 1.6. to make the circuit function well. After that, perform a simulation to double-check your selection.

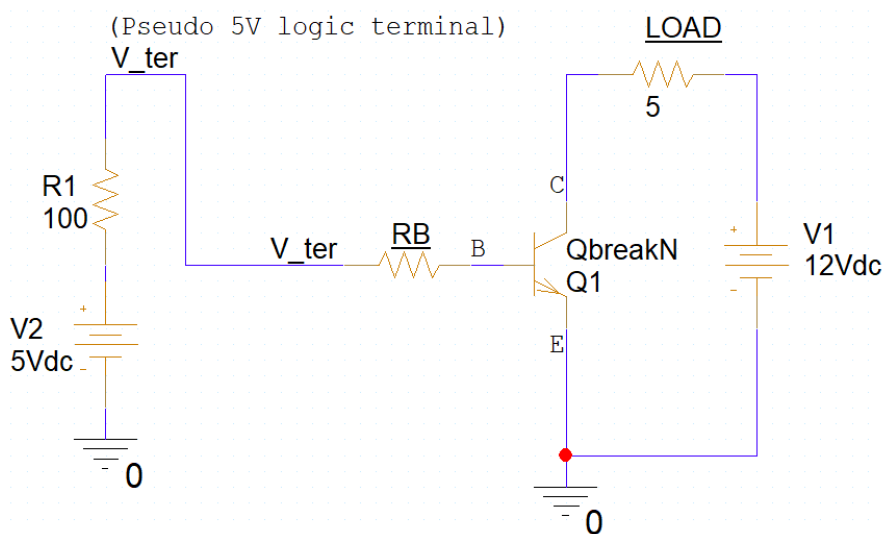


Figure 1.6: Select a resistor available in the market for R_B

3.4.1 Theory calculations

Notes:

Explanations, formulas, and equations are expected rather than only results.

According to the limits of loads and the transistor:

$$300 \text{ mA} < I_C < 400 \text{ mA}$$

$$3 \text{ mA} < I_B < 4 \text{ mA}$$

When $I_B(\min) = 3 \text{ mA}$:

$$R_B(\max) = \frac{V_{ter} - 0.7}{I_B} - R_1 = \frac{5 - 0.7}{3 \cdot 10^{-3}} - 100 = 1333.33 \text{ (Ohm)}$$

When $I_B(\max) = 4 \text{ mA}$:

$$R_B(\min) = \frac{V_{ter} - 0.7}{I_B} - R_1 = \frac{5 - 0.7}{4 \cdot 10^{-3}} - 100 = 975 \text{ (Ohm)}$$


Therefore: $975 \text{ (Ohm)} < R_B < 1333.33 \text{ (Ohm)}$

$R_B(\text{selected}) = 1000 \text{ (Ohm)}$


3.4.2 Simulation

Your image goes here


$R_B(min) : R_B = 975 \text{ Ohm}$

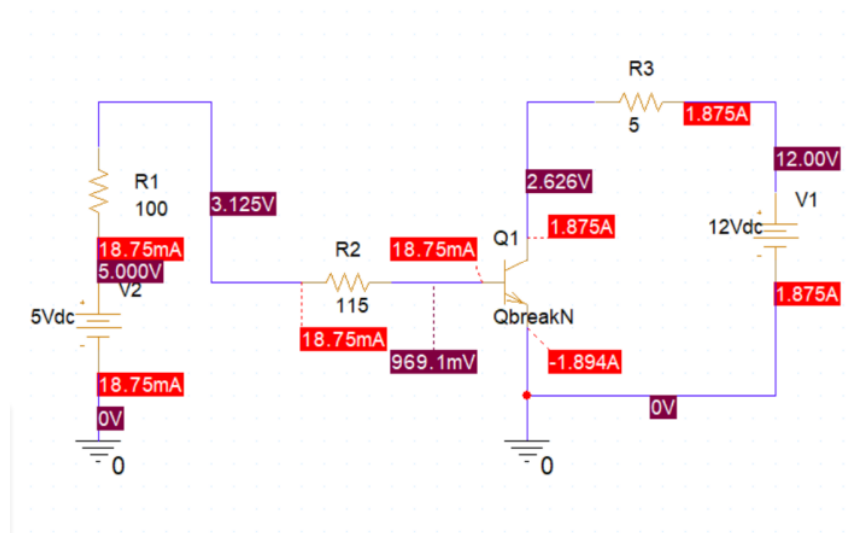

$R_B(max) : R_B = 1333.33 \text{ Ohm}$

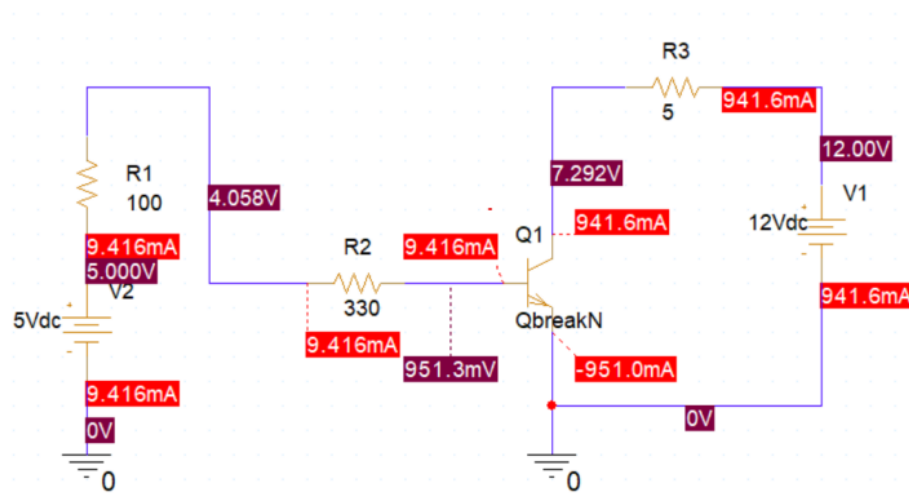

$R_B(selected) : R_B = 1000 \text{ Ohm}$

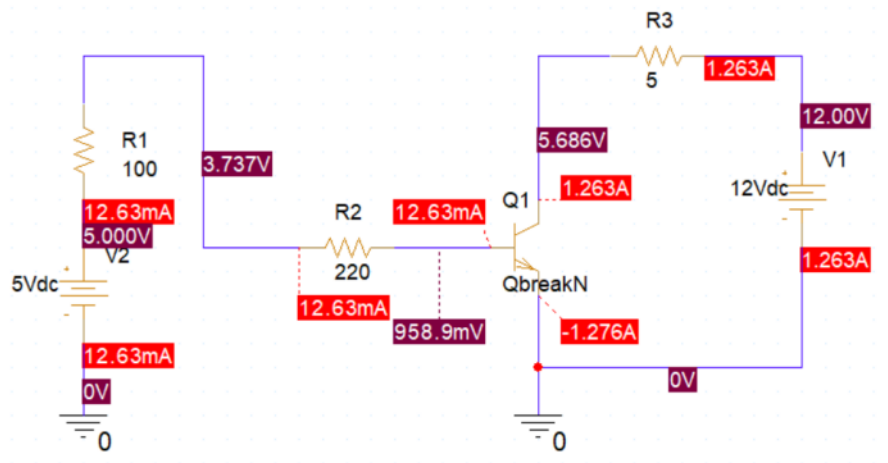

3.4.3 Compare

	Theory				PSpice		
	$R_B(\Omega)$	$V_{BE}(V)$	$I_B \text{ (mA)}$	$I_C \text{ (mA)}$	$V_{BE} \text{ (V)}$	$I_B \text{ (mA)}$	$I_C \text{ (mA)}$
$R_B(min)$	975	0.7	4	400	0.93	3.79	378.8
$R_B(max)$	1333.33	0.7	3	300	0.92	2.8	284.6
$R_B(selected)$	1000	0.7	3.91	390.91	0.93	3.70	370.3

3.5 Simple bias configuration

The circuit given in Figure 1.7 is known as a simple kind of NPN bias configuration. First, students simulate the circuit with two values of R_C , respectively 10 Ohms and 1k Ohms. Then, give your statement on the change of the current I_E and explain the phenomena.


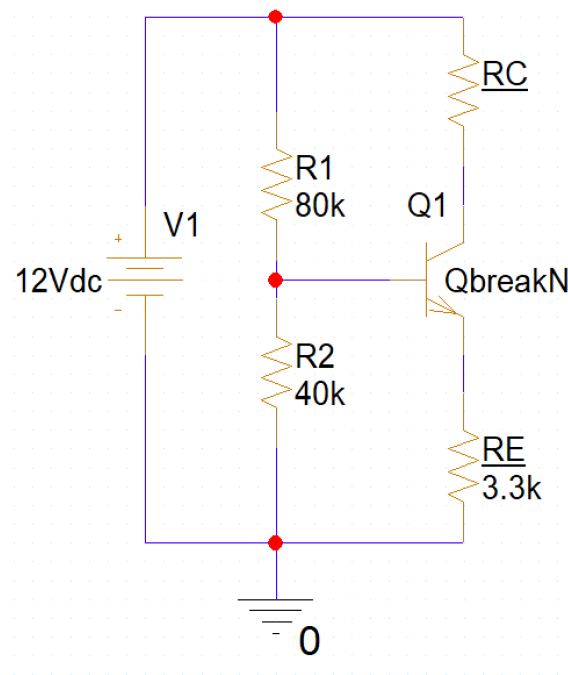


Figure 1.7: Simple bias configuration

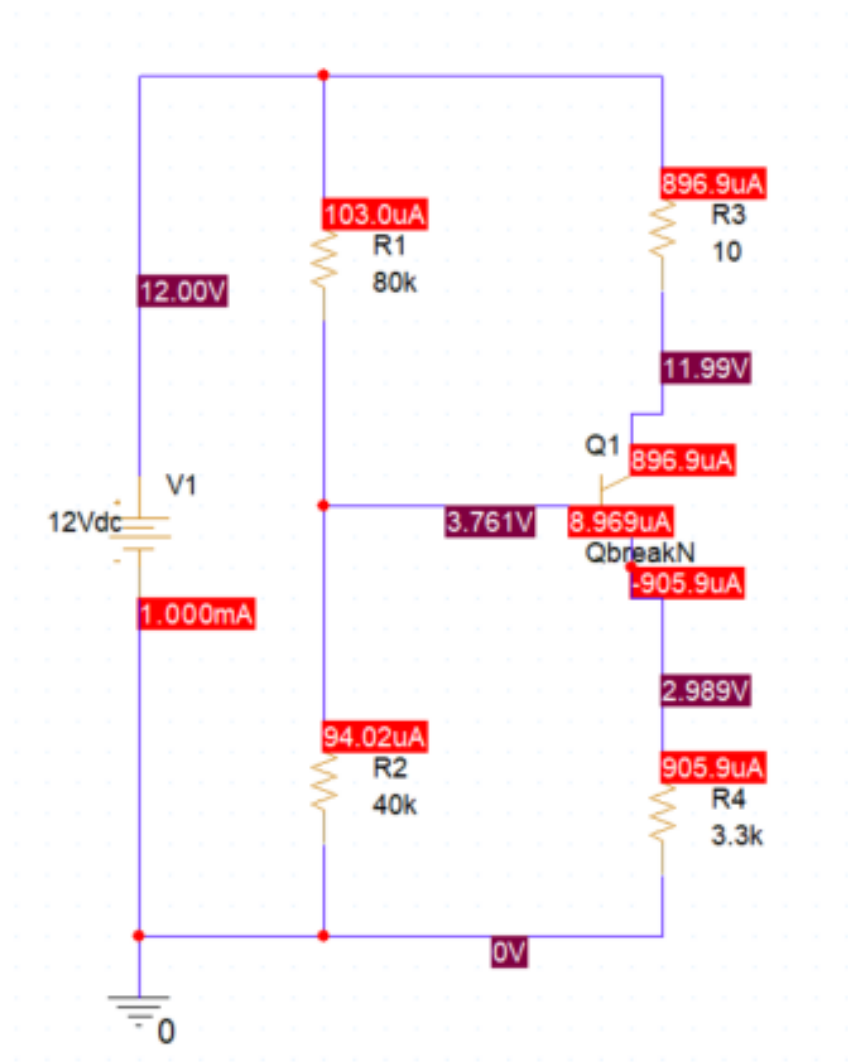
3.5.1 Simulation

Your images go here (2 images)

Step 1: Simulate the circuit with $R_C = 10$ Ohms.



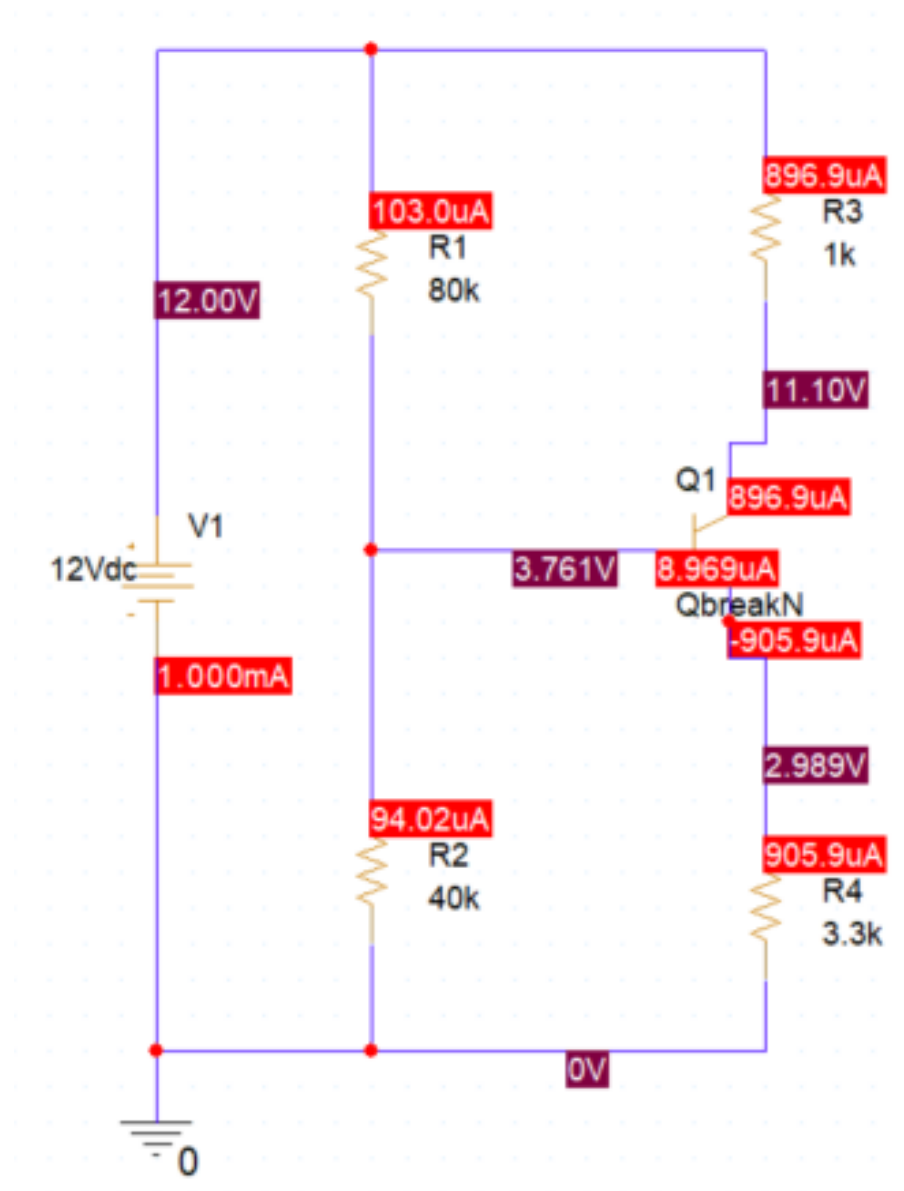Step 2: Simulate the circuit with $R_C = 1\text{k Ohms}$.



3.5.2 Circuit analysis

Conduct some theoretical calculation to explain for the phenomena you have observed from the simulation.

From the simulation results, we can see that the value of I_C remains the same whether R_C is 10 Ohm or 1k Ohm.

We calculate I_C with the default $\beta = 100$:

$$V_{BE} = 0.7 \text{ (V)}; I_E = I_C + I_B \text{ and } I_C = \beta I_B \\ \Rightarrow I_E = (\beta + 1) \cdot I_B$$

$$R_{TH} = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{80k \cdot 40k}{80k + 40k} = \frac{80k}{3} = 26.6667k(\text{Ohm})$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \cdot V_1 = \frac{40k}{40k + 80k} \cdot 12 = 4 \text{ (V)}$$

We have: $V_{TH} = I_B \cdot R_{TH} + V_{BE} + I_E \cdot R_E = I_B \cdot \frac{80}{3} + 0.7 + (\beta + 1) \cdot I_B \cdot 3.3k = 4 \text{ (V)}$

$$\Rightarrow I_B = 9.17 \text{ (}\mu\text{A)}$$

$$I_E = (\beta + 1) \cdot I_B = (100 + 1) \cdot 9.1675 = 925.92 \text{ (}\mu\text{A)}$$

$\Rightarrow I_C$ does not depend on the value of R_c .

3.6 PNP Circuit

Figure 1.8 shows a very typical PNP transistor circuit. Calculate I_B , I_E , and I_C then simulate the circuit to double-check your calculation. Assume the current gain $\beta = 100$.

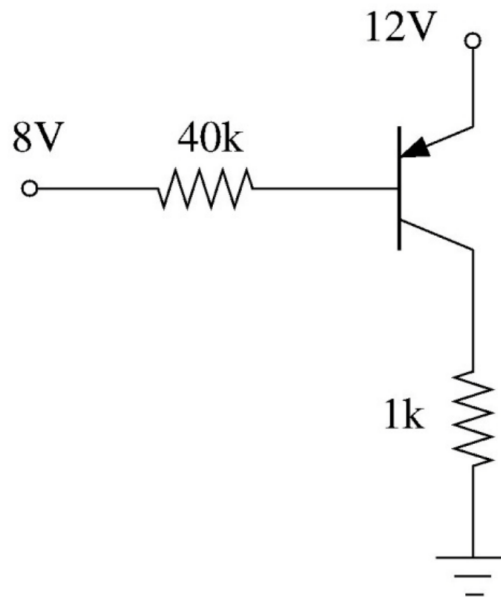


Figure 1.8: A PNP Circuit

3.6.1 Theoretical calculation

Notes:

Explanations, formulas, and equations are expected rather than only results.

$$V_{EB} = 0.7 \text{ (V)}$$

$$8 + V_{EB} + I_B \cdot 40k = 12 \text{ (V)}$$


$$\text{So } I_B = \frac{12 - 8 - V_{EB}}{40} = 0.0825 \text{ (mA)}$$

$$I_C = \beta I_B = 100 \cdot 0.0825 = 8 \text{ (mA)}$$

$$I_E = I_C + I_B = 8.25 + 0.0825 = 8.33 \text{ (mA)}$$

3.6.2 Simulation

Your image goes here

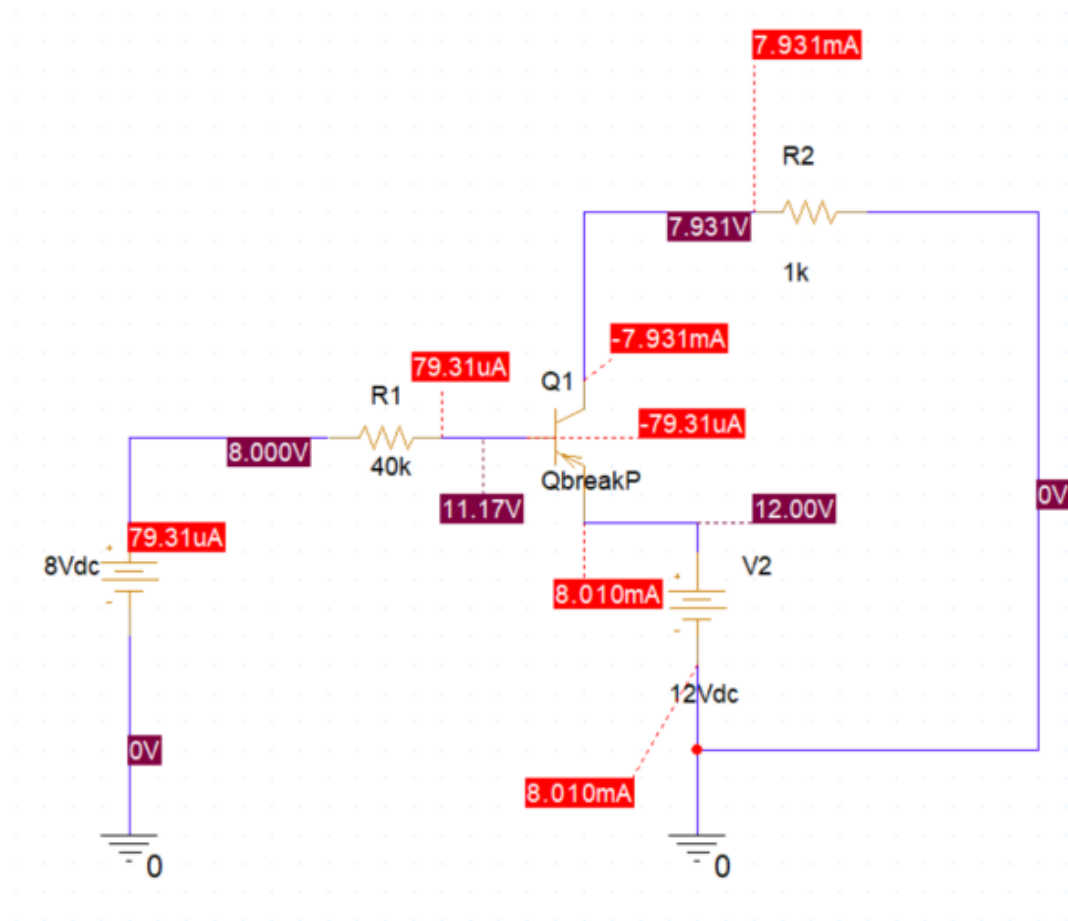

3.6.3 Comparison

I_B (In theory) = 0.08 mA I_B (simulation) = 0.079 mA

I_C (In theory) = 8.25 mA I_C (simulation) = 7.93 mA

I_E (In theory) = 8.33 mA I_E (simulation) = 8.01 mA

3.7 Circuit with NPN and PNP bipolar junction transistors

Give the circuit in Figure 1.9. Calculate the Voltage at all nodes and the current in all branches. Assume the current gain of both transistors is the same at $\beta = 100$. Then perform a simulation and compare the result with the theoretical calculation.

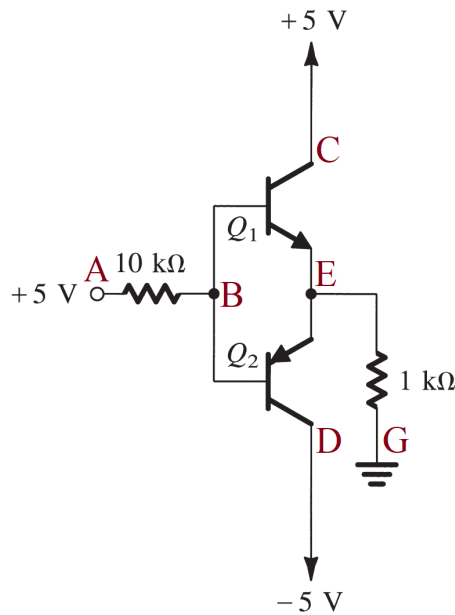


Figure 1.9: Circuit with NPN and PNP bipolar junction transistors

3.7.1 Theoretical calculation

Notes:

Explanations, formulas, and equations are expected rather than only results.

$V_{BE} = V_B - V_E = 0.7V > 0$ so V_E is smaller than V_B , the transistor Q_2 is cut-off.

According to Ohm Law, we have:

$$I_{BE} = I_{AB} = I_B \cdot 10k + 0.7 + I_E \cdot 1k = 5(V)$$

$$I_E = (\beta + 1) \cdot I_B \Rightarrow I_B \cdot 10k + 0.7 + I_B \cdot 101k = 5(V) \Rightarrow I_B = 38.7(\mu A)$$

$$I_C = 3.87(mA)$$


$$I_{EG} = I_B + I_C = 3.91(mA)$$

$$V_E = I_{EG} \cdot 1k = 3.91 \cdot 1k = 3.91(V)$$

$$V_B = 5 - I_B \cdot 10 = 5 - 38.7 \cdot 10^{-3} \cdot 10 = 4.61(V)$$

3.7.2 Simulation

Your image goes here

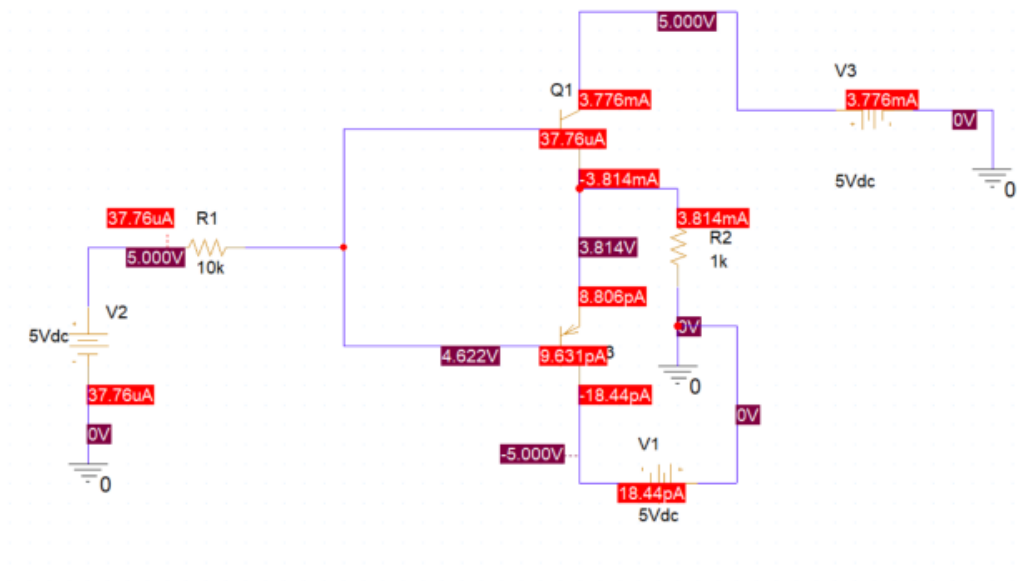

3.7.3 Comparison

Theory Calculation					PSpice Simulation				
I_B	I_C	I_{EG}	V_E	V_B	I_B	I_C	I_{EG}	V_E	V_B
38.7μA	3.87mA	3.91mA	3.91V	4.61V	37.76μA	3.78mA	3.81mA	3.81V	4.62V