

CO2037 - Electrical Electronic Circuits

Diode and Its Applications



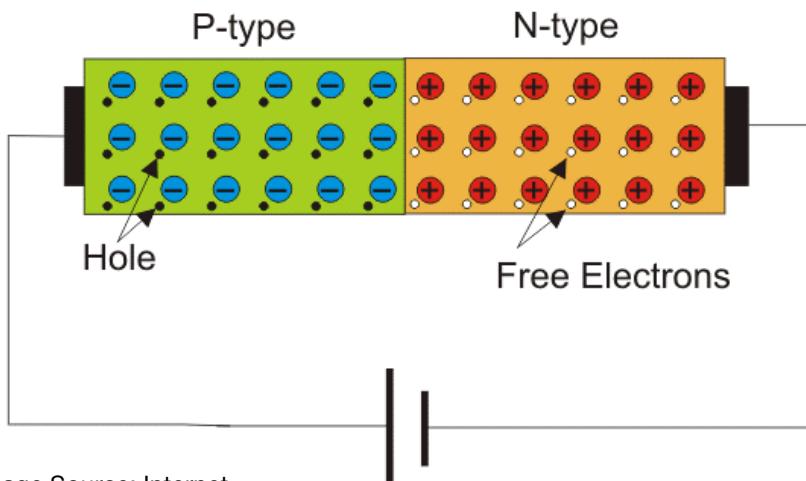


Image Source: Internet

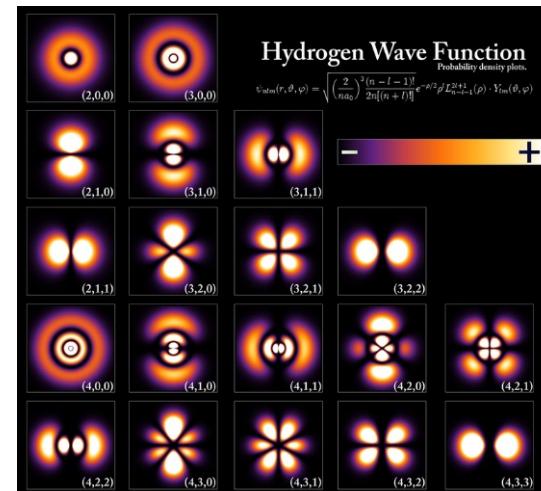


Diode and Its Applications

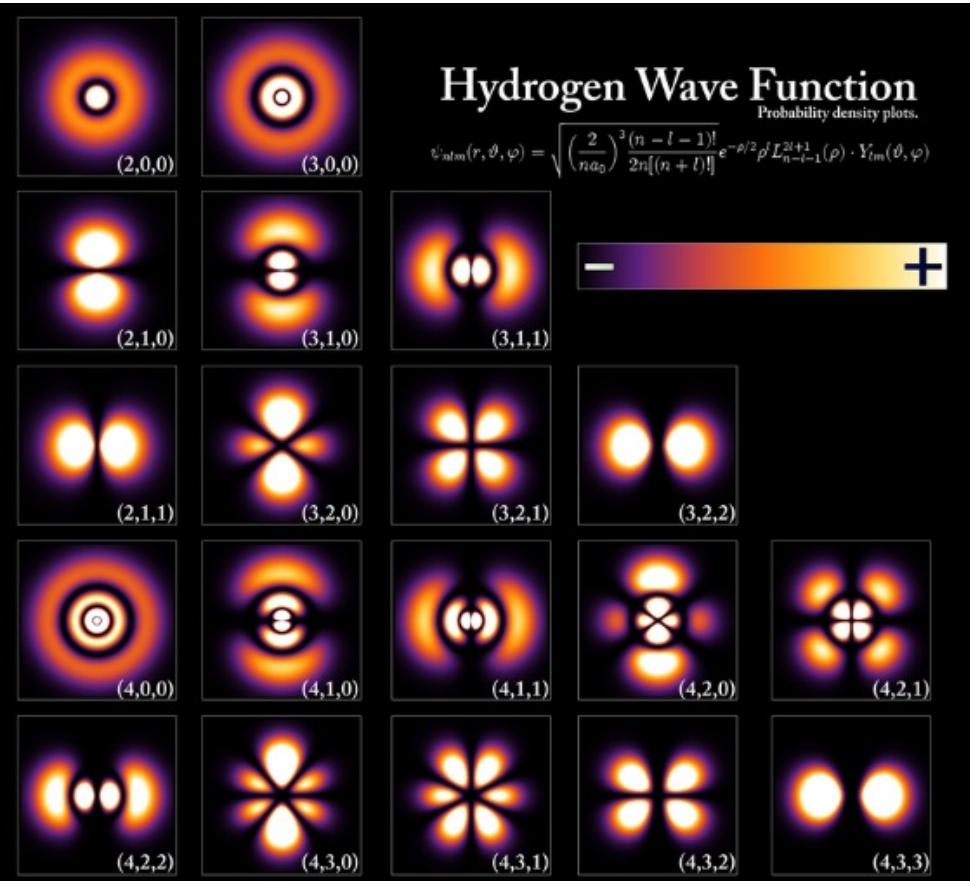- Introduction to semiconductor
- Diode
- Applications




Semiconductor

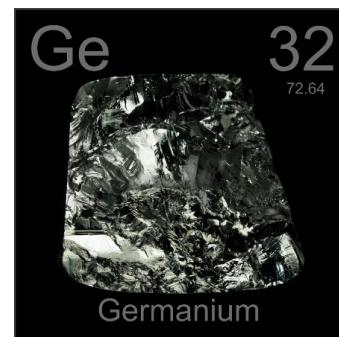- Semiconductors are a special class of elements having a conductivity between that of a good conductor and that of an insulator.
- Two classes: **single-crystal** and **compound**
- The three semiconductors used most frequently in the construction of electronic devices are **Ge**, **Si**, and **GaAs**.



Germanium (Ge)

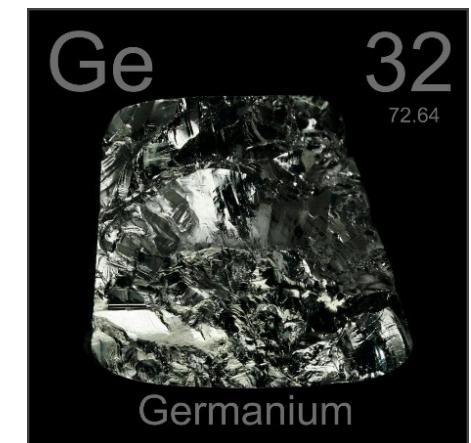- The discovery of the diode in 1939 and the transistor in 1947 germanium was used almost exclusively
- Advantages
 - Easy to find
 - Fairly large quantities
 - Easy to refine to obtain very high levels of purity
- Disadvantage
 - Sensitivity to changes in temperature



Silicon (Si)

- 1954 the first silicon transistor was introduced
- Advantages
 - Less temperature sensitive
 - The most abundant materials on earth
 - High levels of purity
- Disadvantage
 - Sensitive to issues of speed.





Gallium Arsenide (GaAs)

- The first GaAs transistor in the early 1970s.
- New transistor had speeds of operation up to five times that of Si.
- GaAs was more difficult to manufacture at high levels of purity, was more expensive.
- Today, it is often used as the base material for new high-speed, very large scale integrated (VLSI) circuit designs.




Diode

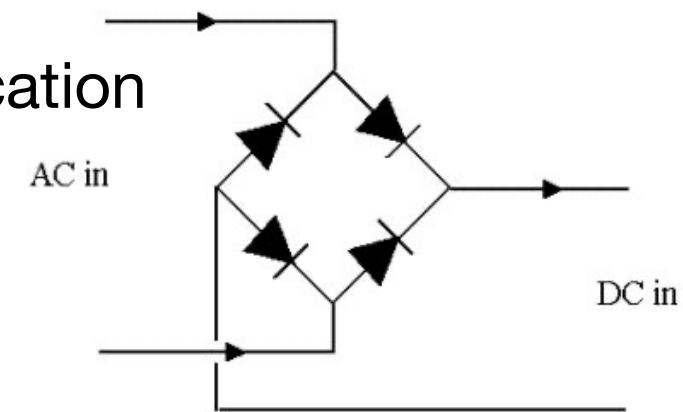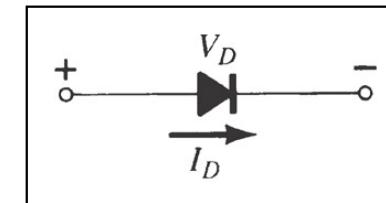- The diode is the simplest and most fundamental non-linear circuit element
- Like a resistor, it has two terminals
- Unlike a resistor, it has a non-linear current-voltage characteristics.
- Its use in rectifiers is the most common application




Diode

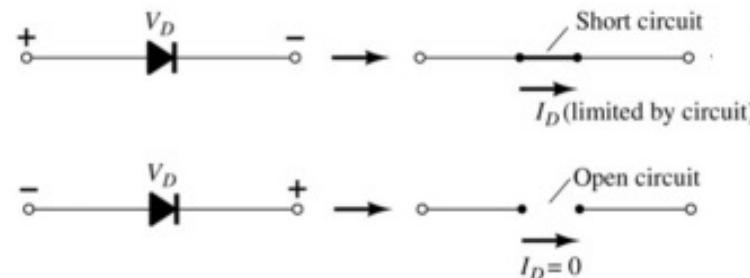
- Diode is an electric device which allows current to flow only in one direction.



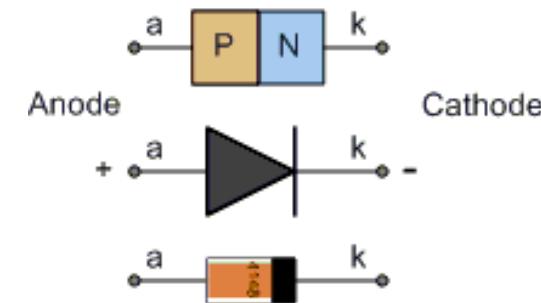- The voltage applied to the semi conductor diode is referred to as bias voltage
- There are two types of bias voltage
 - Forward biased
 - Reversed biased




PN Junction and Diode (Video)

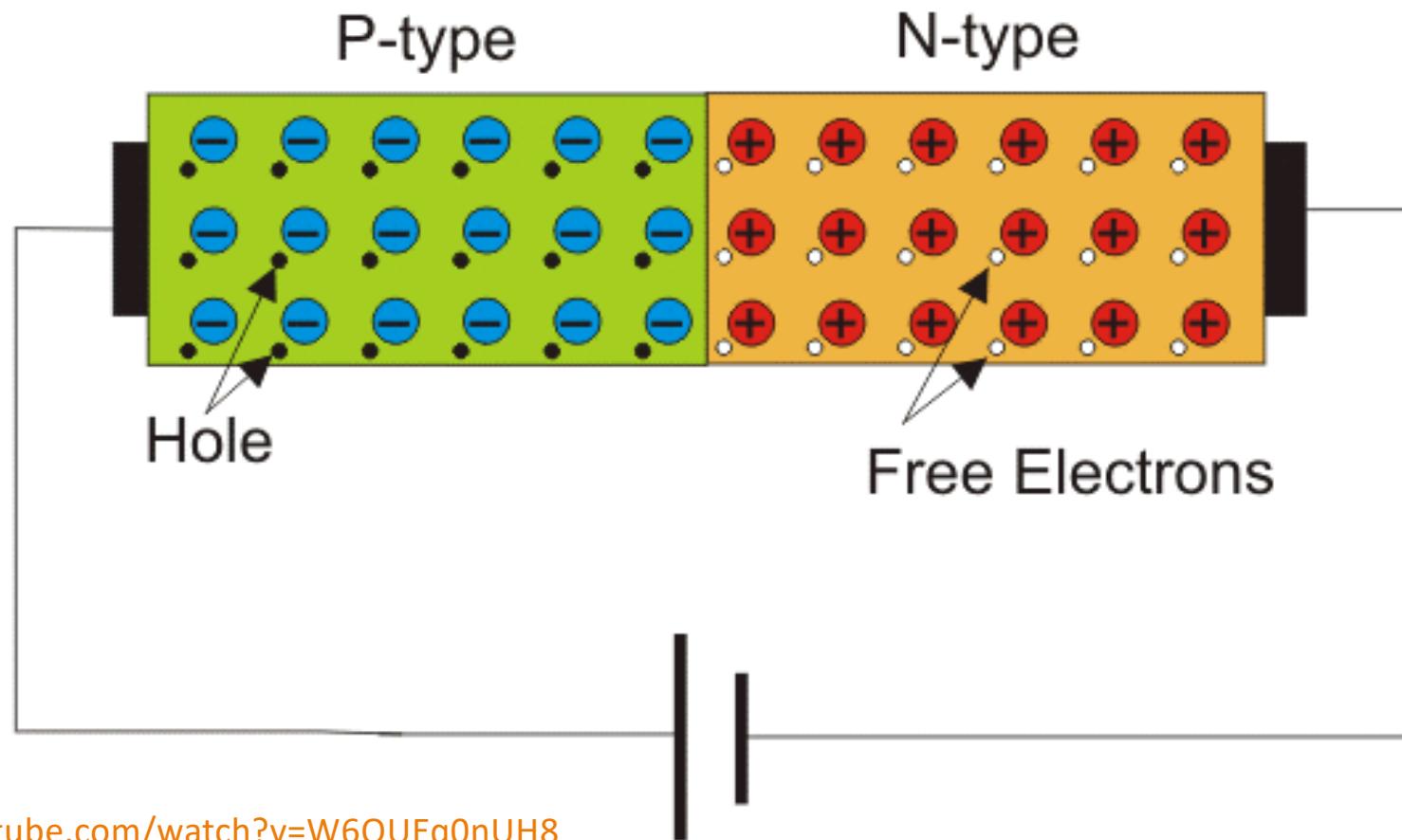

<https://www.youtube.com/watch?v=W6QUEq0nUH8>




Diodes

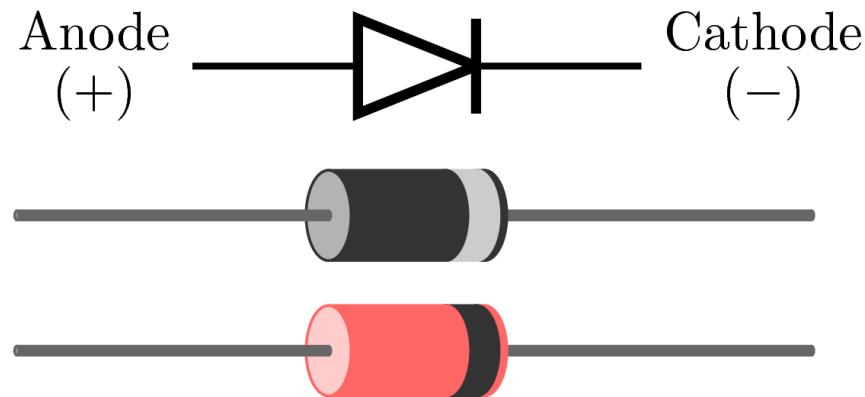

- Diode is composed of **P** and **N** semiconductors
- Diode is **ON** when $V_{AC} \geq 0.7V$
- Diode is **OFF** when $0 \geq V_{AC} \geq -1000V$
- Out of this range, diode is broken


Diode – No Bias

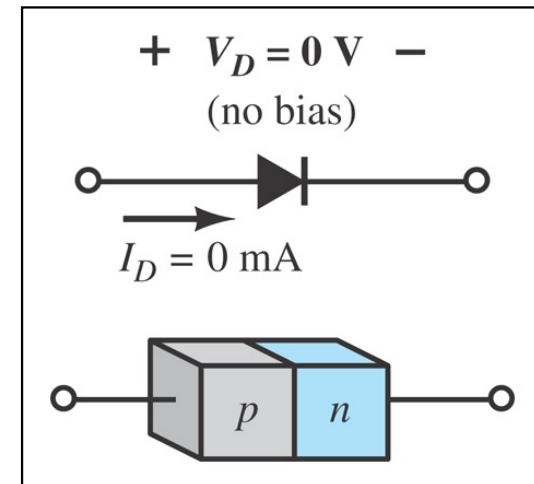- No external voltage is applied: $V_D = 0 \text{ V}$
- There is no diode current: $I_D = 0 \text{ A}$
- Only a modest depletion region exists





Diode – Forward Bias

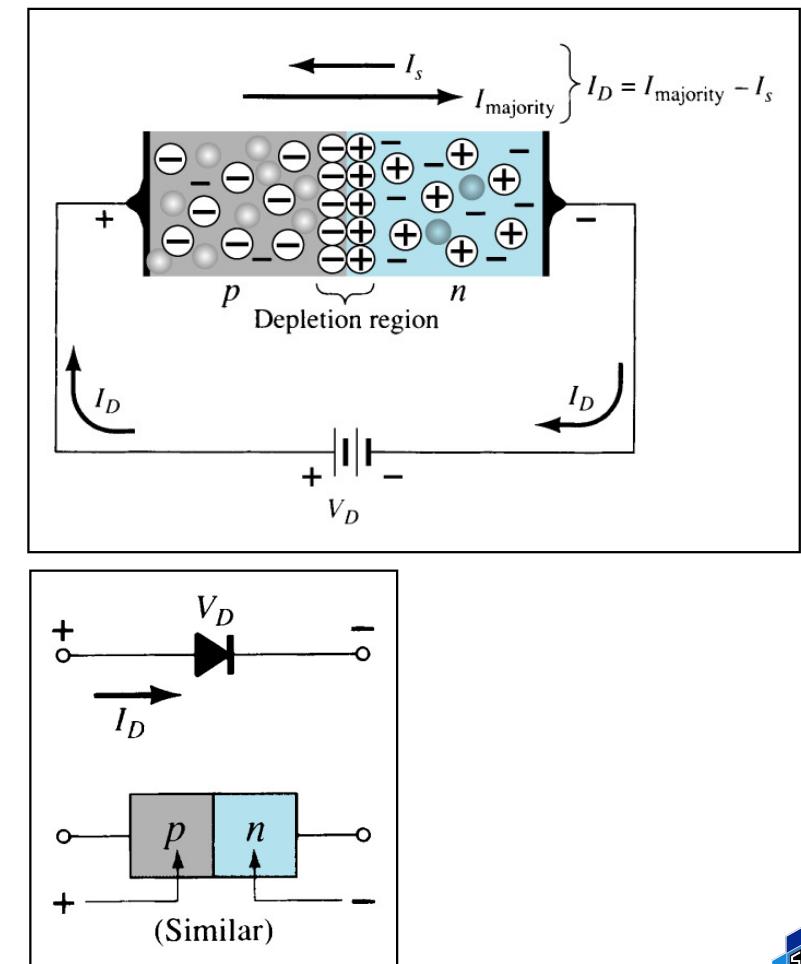- External voltage is applied across the *p-n* junction in the same polarity as the *p*- and *n*-type materials.
- The forward voltage causes the depletion region to narrow.
- The electrons and holes are pushed toward the *p-n* junction.
- The electrons and holes have sufficient energy to cross the *p-n* junction



Diode – Reverse Bias

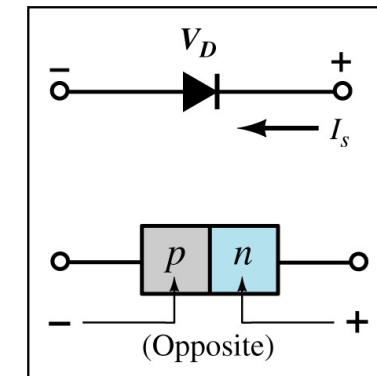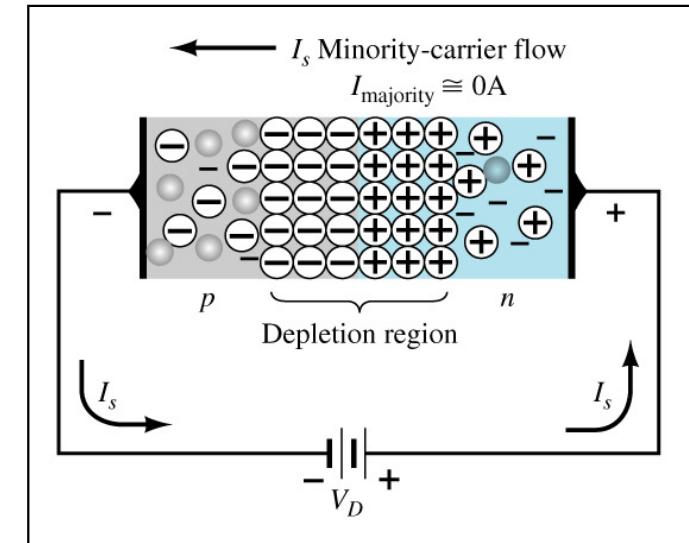- External voltage is applied across the p - n junction in the opposite polarity of the p - and n -type materials.
- The reverse voltage causes the depletion region to widen.
- The electrons in the n -type material are attracted toward the positive terminal of the voltage source.
- The holes in the p -type material are attracted toward the negative terminal of the voltage source.



Diode Equivalent Circuit


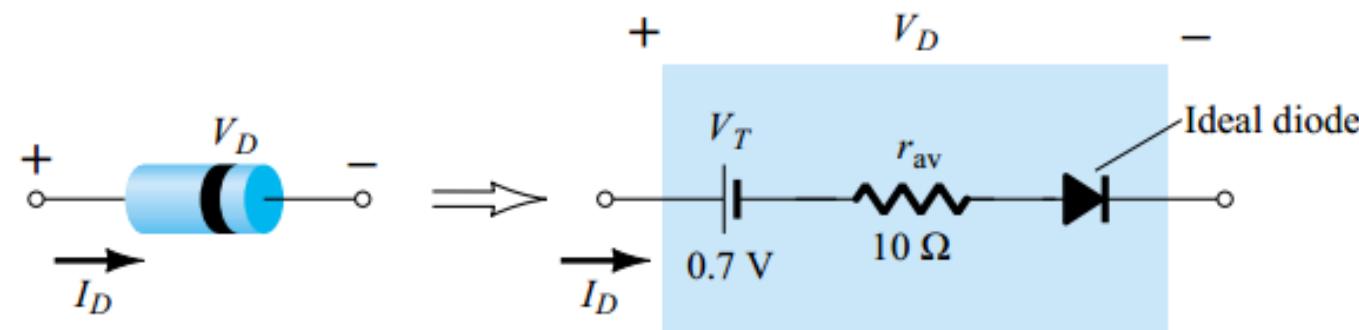


Figure 1.32 Components of the piecewise-linear equivalent circuit.


Ideal Diode Model

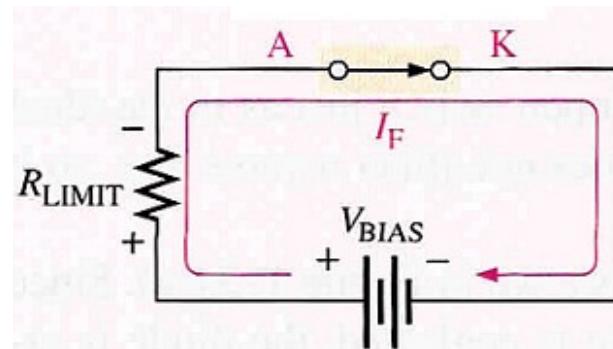- Works as a switch
 - Forward bias (switch is close)
 - Reverse bias (switch is open)
- Threshold battery voltage and internal resistance are ignored.



$$I_F = \frac{V_{BIAS}}{R_{LIMIT}}$$

Forward bias

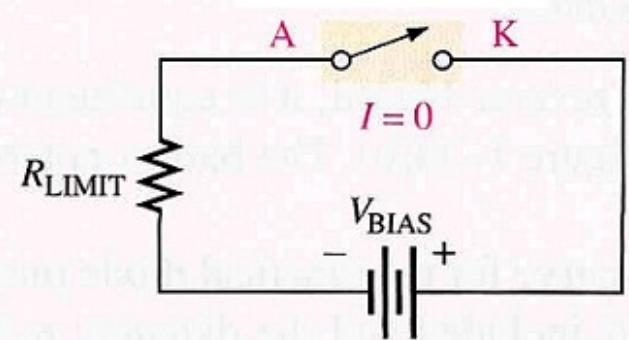


Reverse bias




Practical Diode Model
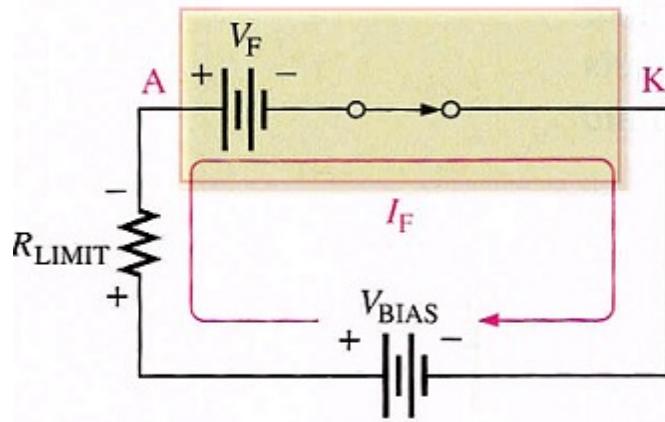
$$I_F = \frac{V_{BIAS} - V_F}{R_{LIMIT}}$$



Forward bias

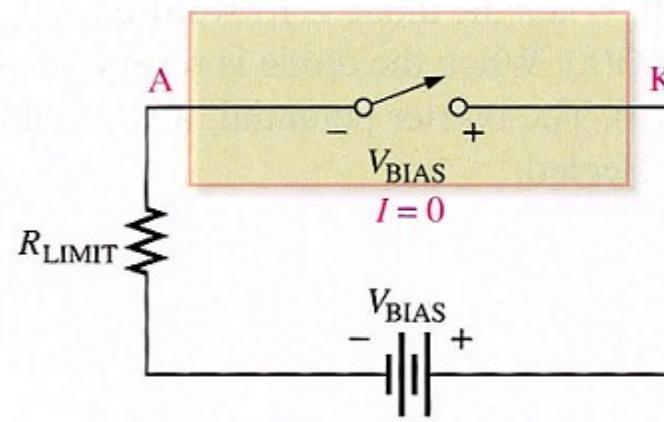

Reverse bias


■ Constants

- Silicon Diode: $V_F = 0.7V$ ($V_F = V_{BIAS}$ if $V_{BIAS} < 0.7V$)
- Germanium Diode: $V_F = 0.3V$ ($V_F = V_{BIAS}$ if $V_{BIAS} < 0.3V$)




Complete Diode Model
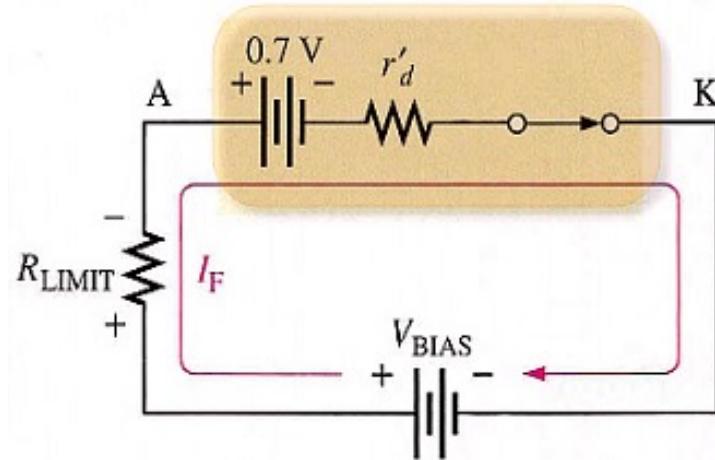
$$I_F = \frac{V_{BIAS} - 0,7\text{ V}}{R_{LIMIT} + r'_d}$$



Forward bias
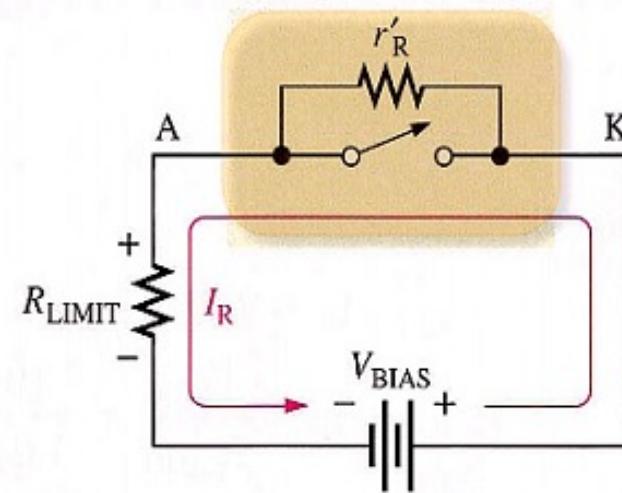
$$I_R = \frac{V_{BIAS}}{R_{LIMIT} + r'_R}$$





Reverse bias

Load-Line Analysis


The load line plots all possible combinations of diode current (I_D) and voltage (V_D) for a given circuit. The maximum I_D equals E/R , and the maximum V_D equals E .

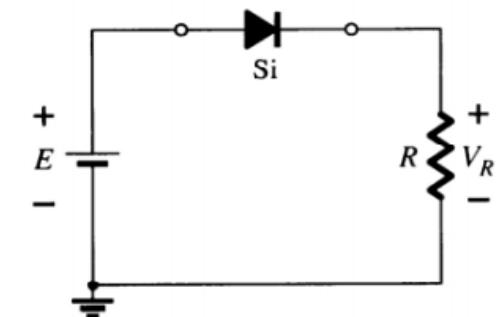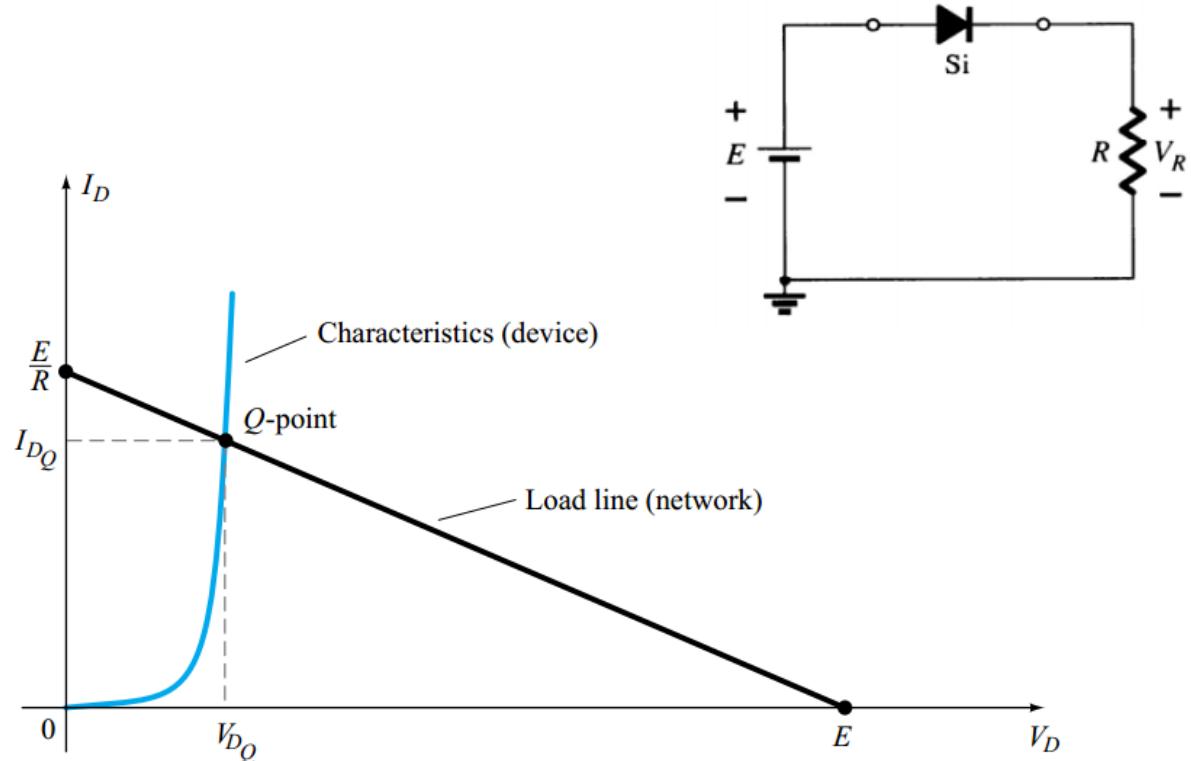The point where the load line and the characteristic curve intersect is the Q-point, which identifies I_D and V_D for a particular diode in a given circuit.





Diode Symbol and Packaging

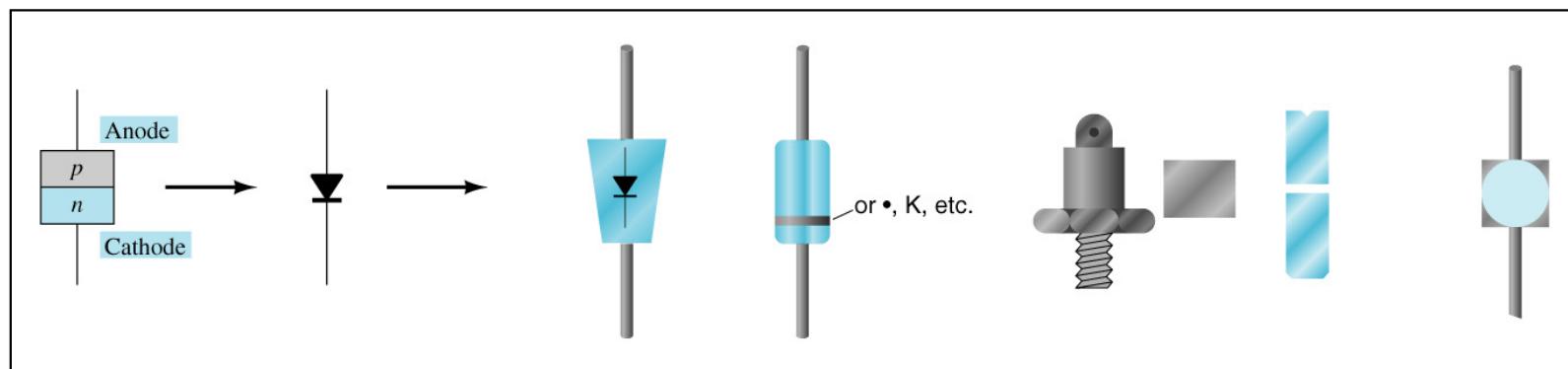- The anode is abbreviated A
- The cathode is abbreviated K




Diode Testing

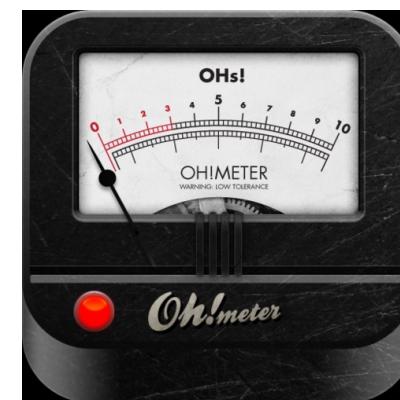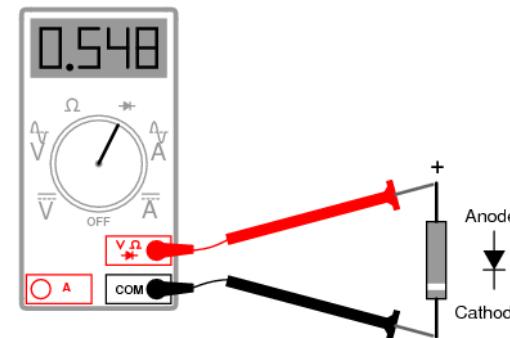- Diodes are commonly tested using one of these types of equipment:
 - Diode checker
 - Ohmmeter
 - Curve tracer



Diode Checking using OPAM

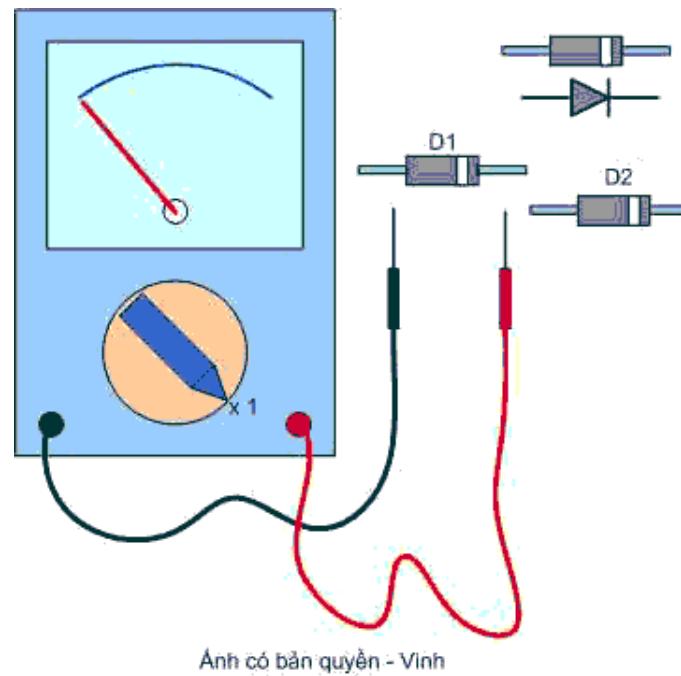


- Black – Anode (Red – Cathode): Cursor moves ON
- Reverse connection: Cursor stops




Diode Checker

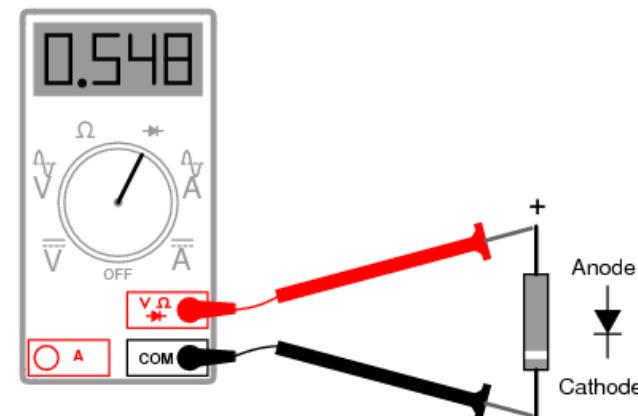- Many digital multimeters have a diode checking function. The diode should be tested out of circuit.
- A normal diode exhibits its forward voltage:
 - Gallium arsenide ≈ 1.2 V
 - Silicon diode ≈ 0.7 V
 - Germanium diode ≈ 0.3 V




Ohmmeter

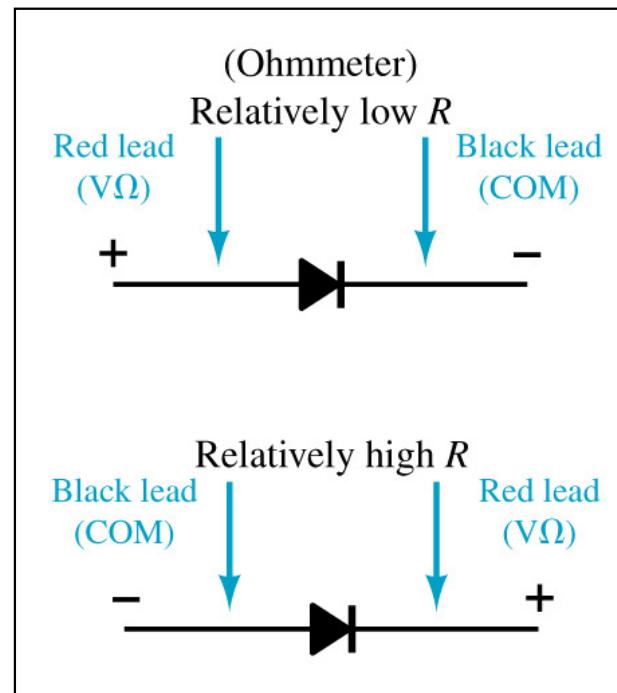- An ohmmeter set on a low Ohms scale can be used to test a diode. The diode should be tested out of circuit.





Curve Tracer

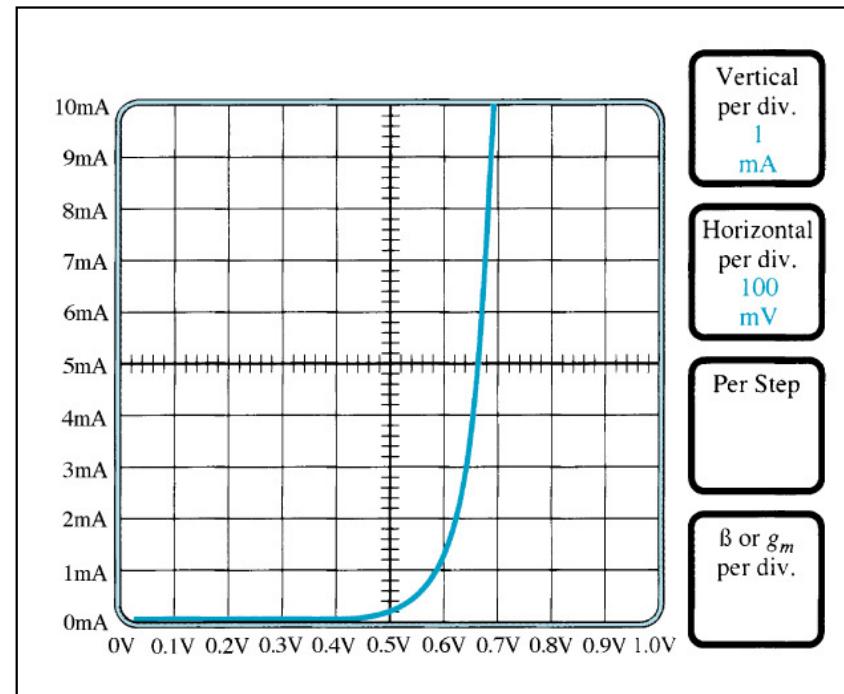- A curve tracer displays the characteristic curve of a diode in the test circuit. This curve can be compared to the specifications of the diode from a data sheet.




Other Types of Diodes

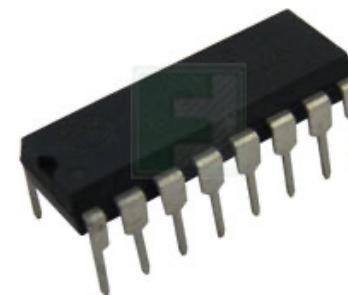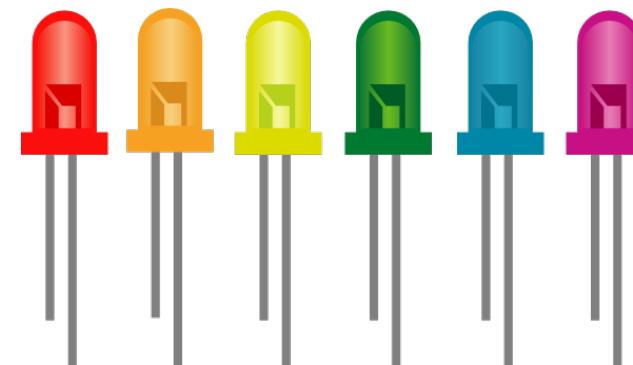- There are several types of diodes besides the standard $p-n$ junction diode. Three of the more common are:
 - Zener diodes
 - Light-emitting diodes
 - Diode arrays





Zener Diode

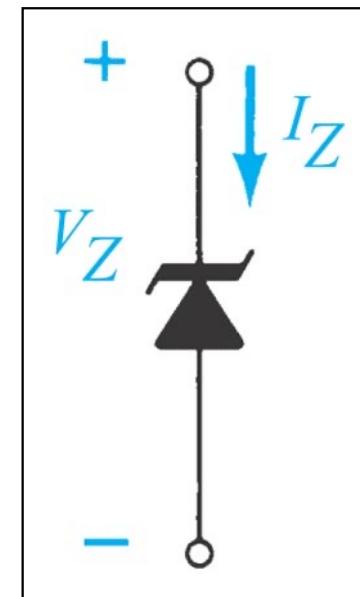- A **Zener diode** is one that is designed to safely operate in its zener region; i.e., biased at the Zener voltage (V_Z).
- Common zener diode voltage ratings are between 1.8 V and 200 V



Light-Emitting Diode (LED)

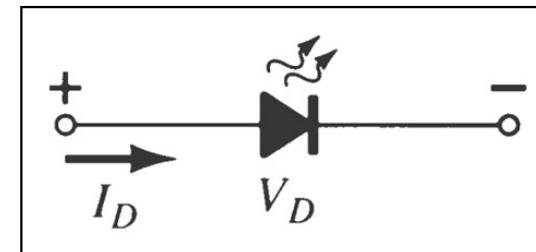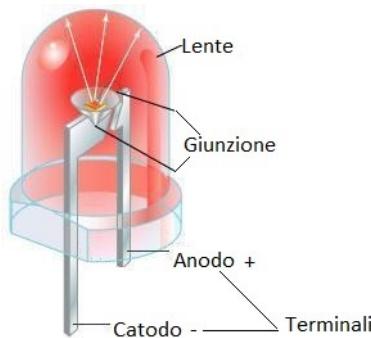
- An **LED** emits light when it is **forward biased**, which can be in the infrared or visible spectrum.
- The forward bias voltage is usually in the range of 2 V to 3 V.





Diode Arrays

- Multiple diodes can be packaged together in an integrated circuit (IC).
- A variety of diode configurations are available.


Common Anode

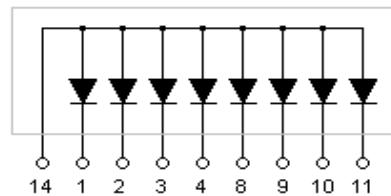

Common Cathode

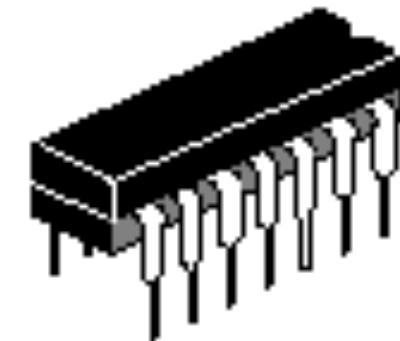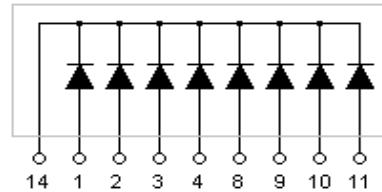

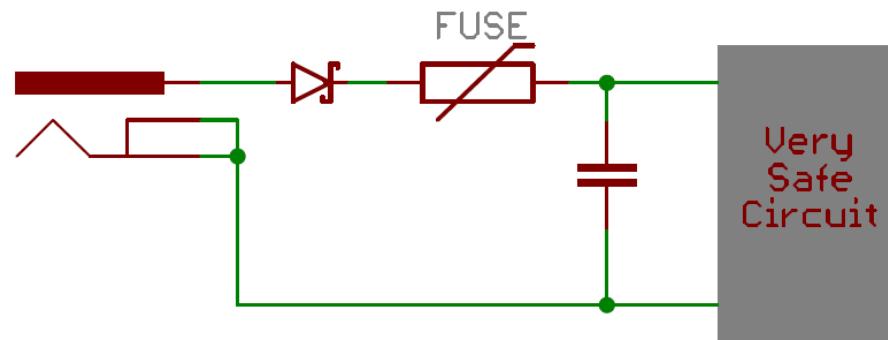
Diode Application - Reverse Current Protection






- **Mandatory design** for any system
- Drawback: around 0.7V loss because of the forward voltage drop.
 - **Schottky diodes** an excellent choice for reverse protection diodes.

Diode Application – Reverse Current Protection

- SIM800L: 4.3V


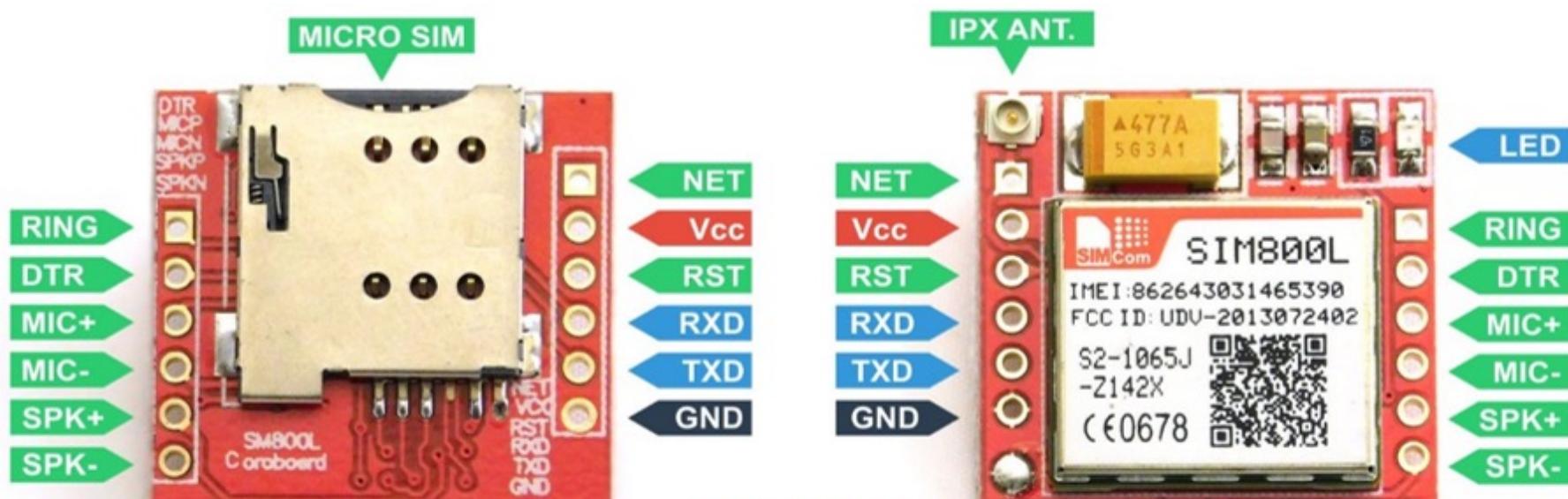


DC Adapter Circuits

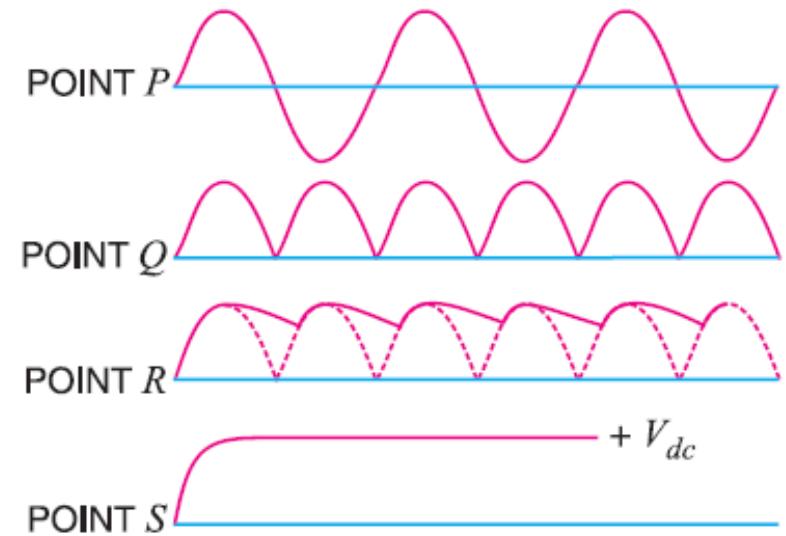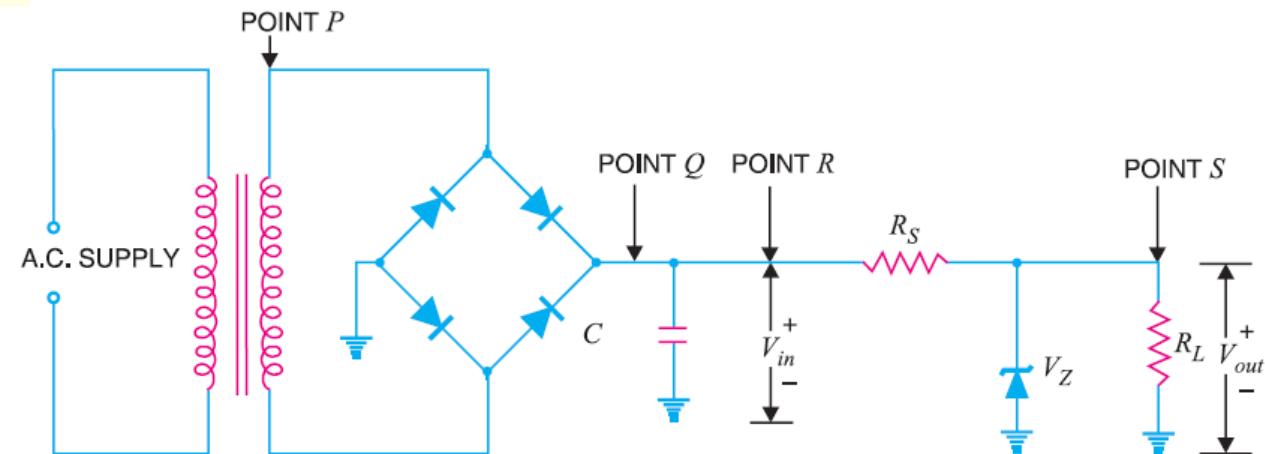
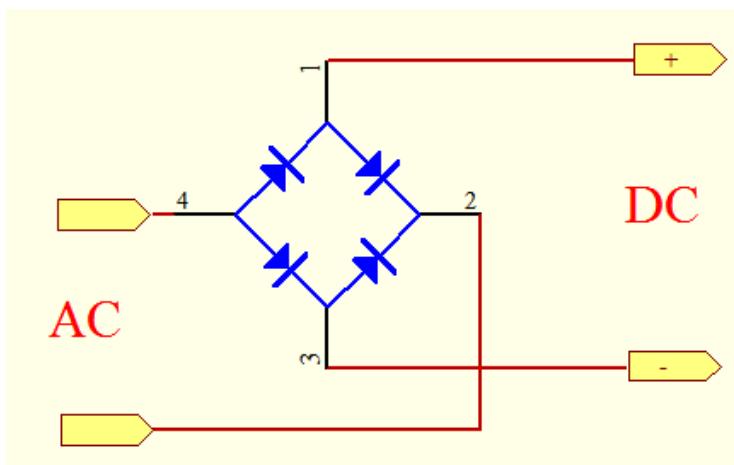


Diode Application - Rectifier

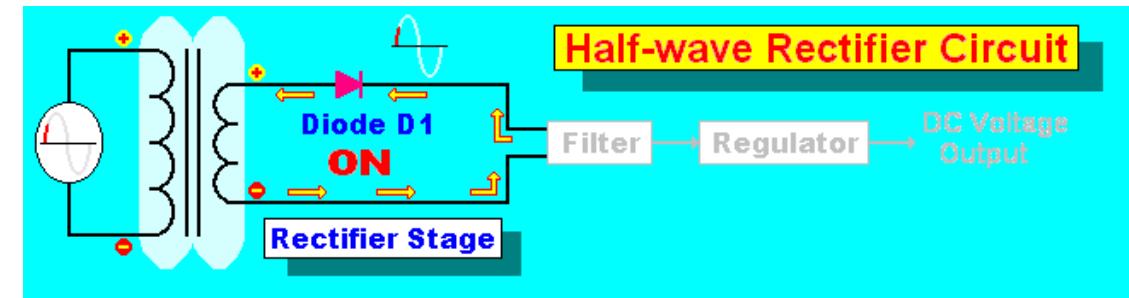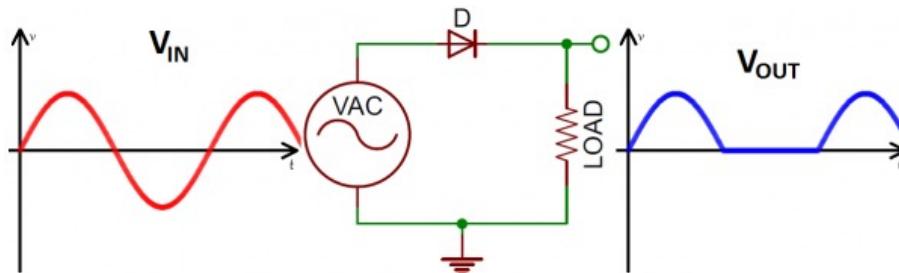
- Convert **Alternating Current (AC)** to **Direct Current (DC)**
 - Half wave rectifier




- Full wave rectifier

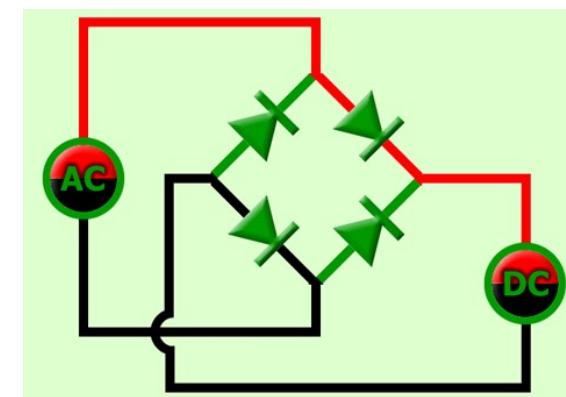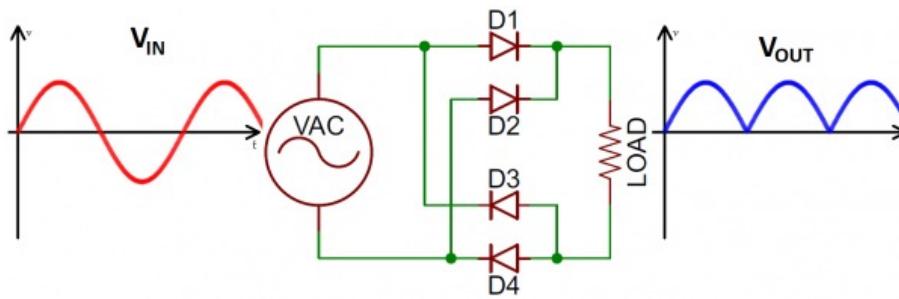

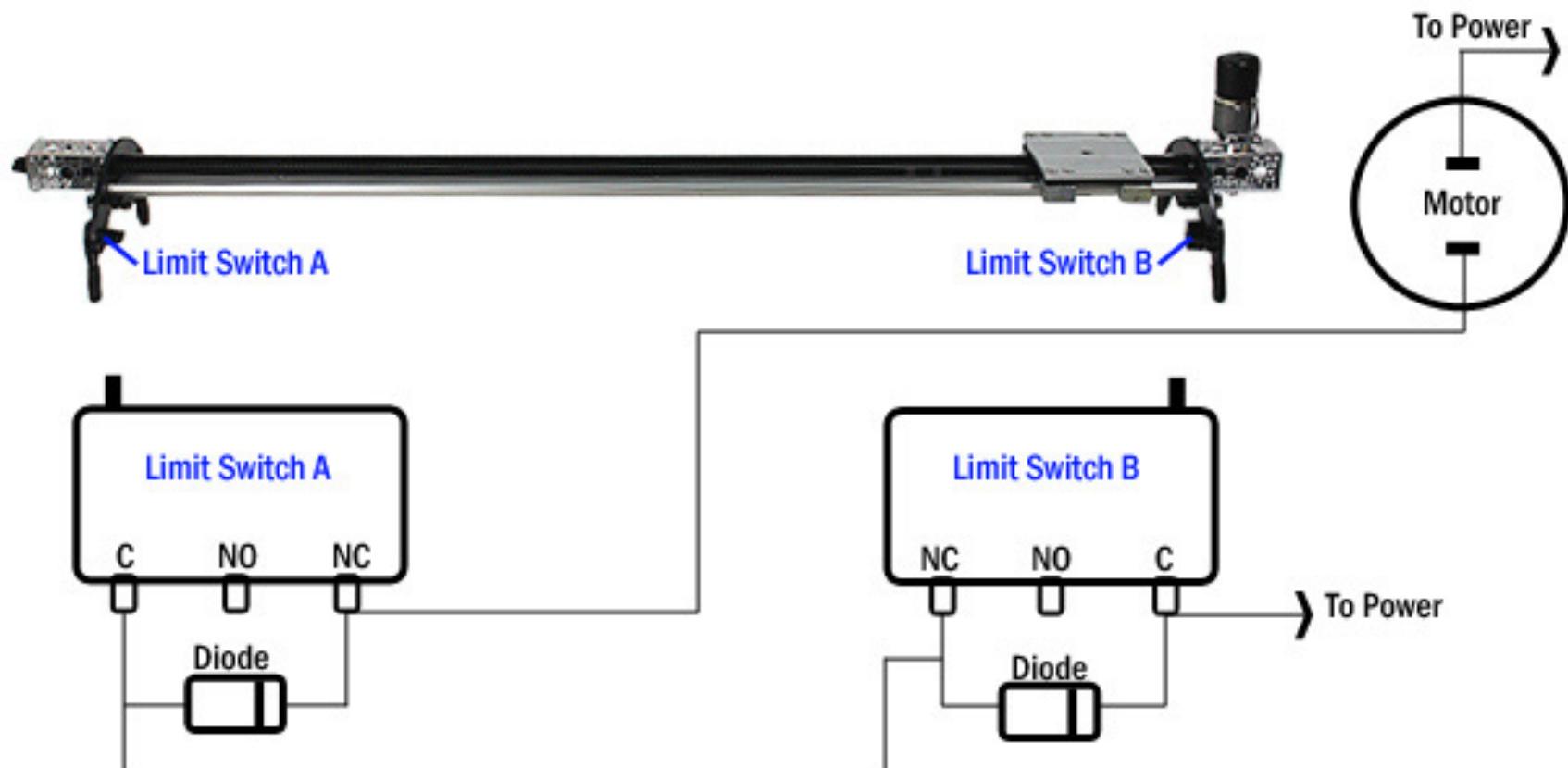
Diode Application - Limit Switch Application



Diode Application - Logic Gates

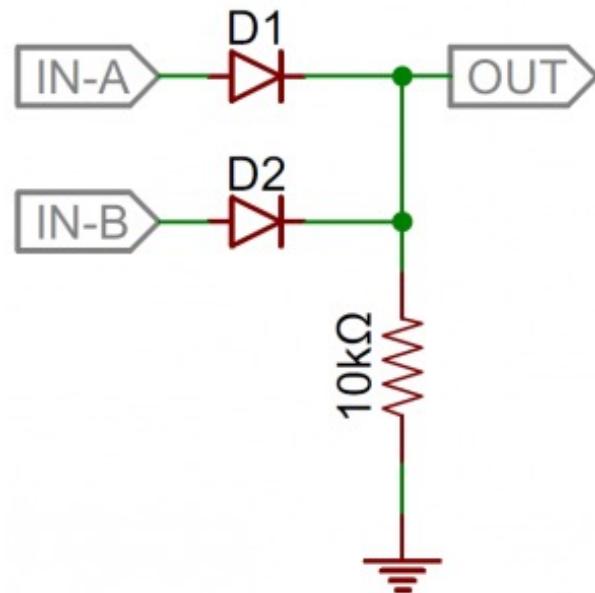


- OR

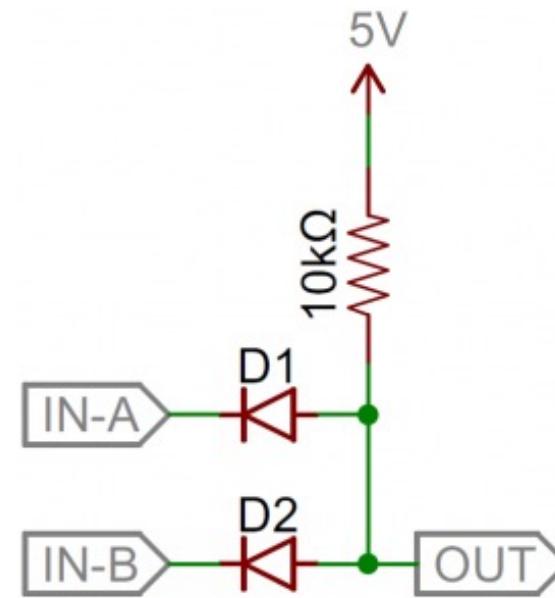

- AND

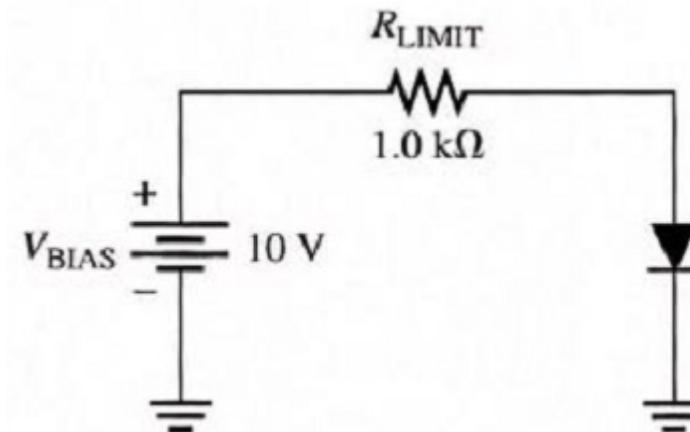Exercise 1

- Given circuit
 - Forward bias voltage $V_F = 0.7V$
 - Internal resistance $r'_d = 10\Omega$
- Determine V_F , I_F and V_{RLIMIT} for three diode models
 - Ideal diode model
 - Practical diode model
 - Complete diode model




Solution

- Ideal diode model

$$V_F = 0 \text{ V}$$

$$I_F = \frac{V_{BIAS}}{R_{LIMIT}} = \frac{10 \text{ V}}{1 \text{ k}\Omega} = 10 \text{ mA}$$
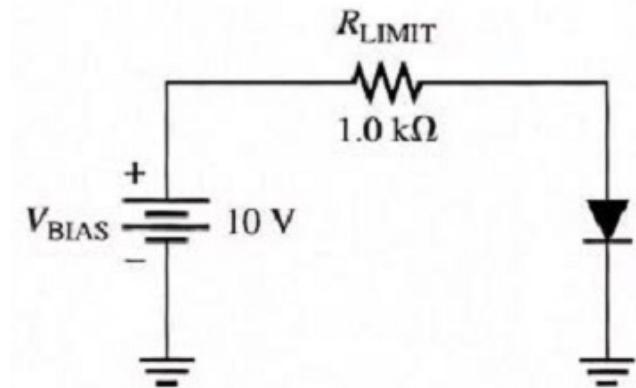
$$V_{R_{LIMIT}} = I_F \cdot R_{LIMIT} = (10 \text{ mA}) \cdot (1 \text{ k}\Omega) = 10 \text{ V}$$



- Practical diode model

$$V_F = 0,7 \text{ V}$$

$$I_F = \frac{V_{BIAS} - V_R}{R_{LIMIT}} = \frac{10 \text{ V} - 0,7 \text{ V}}{1 \text{ k}\Omega} = 9,3 \text{ mA}$$

$$V_{R_{LIMIT}} = I_F \cdot R_{LIMIT} = (9,3 \text{ mA}) \cdot (1 \text{ k}\Omega) = 9,3 \text{ V}$$

- Complete diode model


$$I_F = \frac{V_{BIAS} - 0,7}{R_{LIMIT} + r'_d} = \frac{10 \text{ V} - 0,7 \text{ V}}{1 \text{ k}\Omega + 10 \Omega} = \frac{9,3 \text{ V}}{1010 \Omega} = 0,00921 \text{ A} = 9,21 \text{ mA}$$

$$V_F = 0,7 \text{ V} + r'_d \cdot I_F = 0,7 \text{ V} + (10 \Omega) \cdot (9,21 \text{ mA}) = 792 \text{ mV}$$


$$V_{R_{LIMIT}} = I_F \cdot R_{LIMIT} = (9,21 \text{ mA}) \cdot (1 \text{ k}\Omega) = 9,21 \text{ V}$$

Exercise 2

- Analyze the circuit by using the diode practical model.
- $V_S = 5V$ and the current (I_D) in the circuit is $1mA$.
- What is the value of R_L .
- The dropdown voltage of the diode is $0.7V$

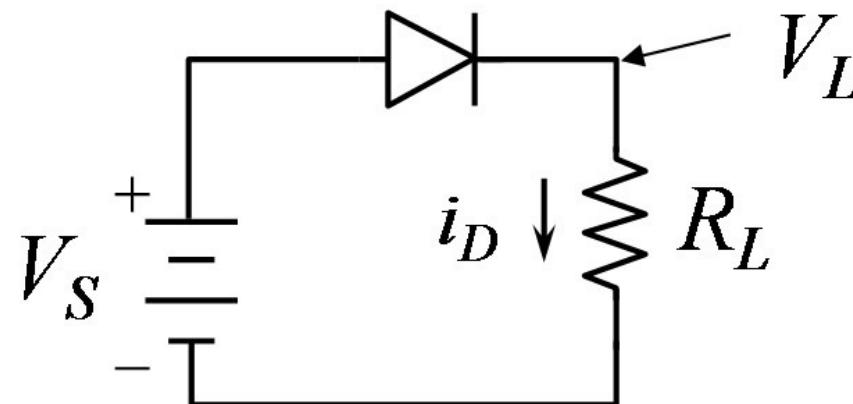


Exercise 3

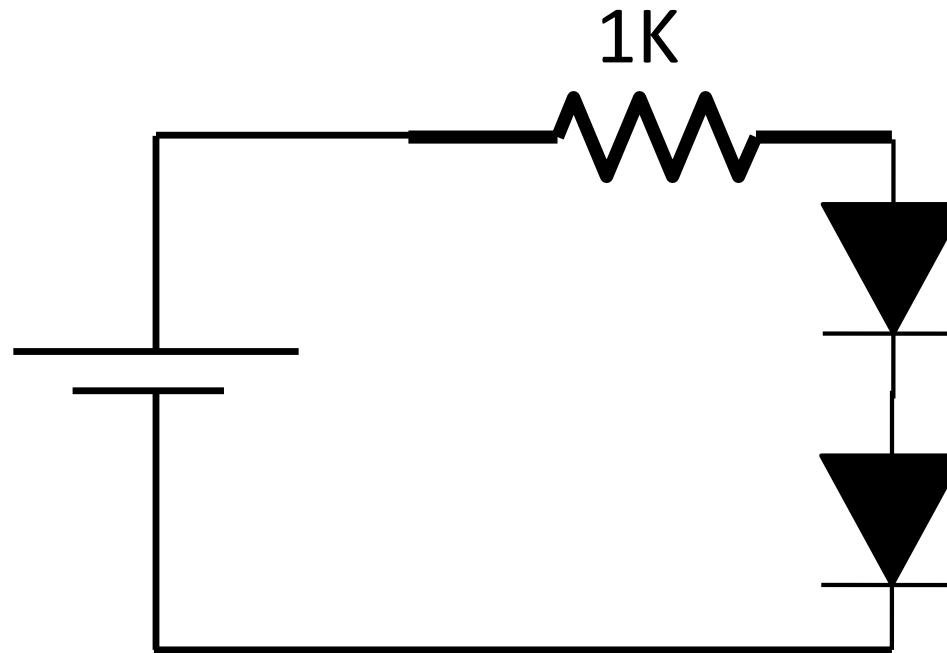

- The voltage supply is 9V, the dropdown voltage of each diode is $V_F=0.7V$ and $r_d=10\text{ ohm}$. Determine the current in the circuit.

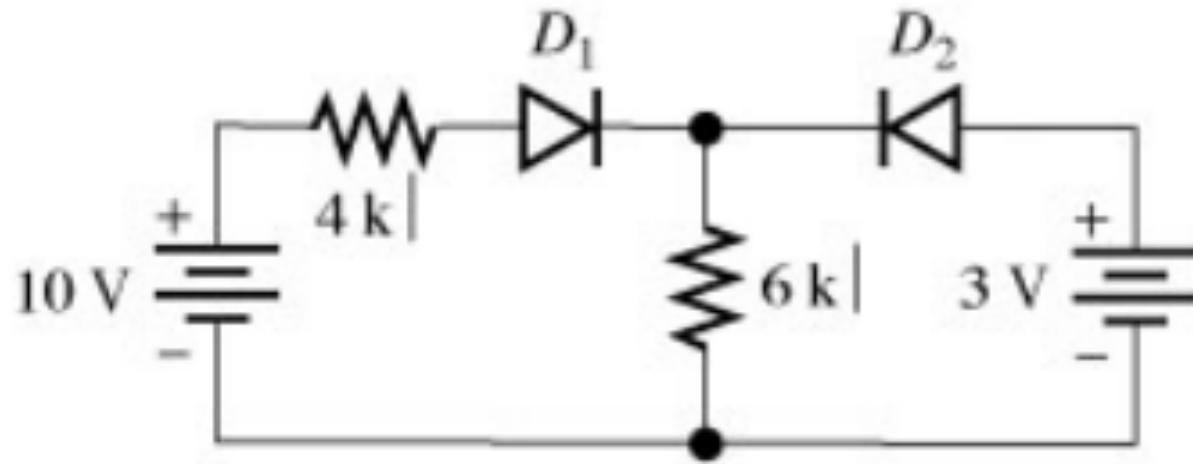
Exercise 4

- Analyze the circuit using ideal diode model




Solution (Ex. 4)

- Assume that D1 is OFF and D2 is ON

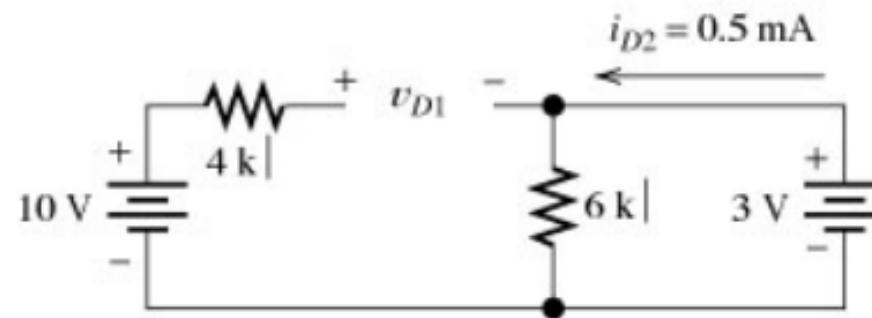


- Assume that D1 is ON and D2 is OFF

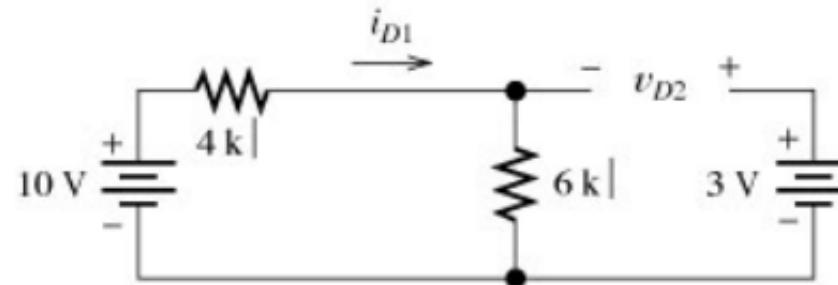

Solution (Ex. 4)

- Assume that both D1 and D2 are OFF

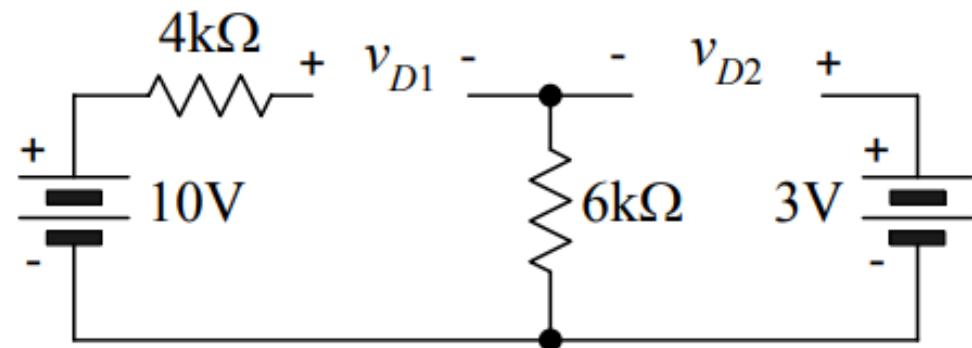


- Assume that both D1 and D2 are ON

$$i_{D1} + i_{D2} = \frac{3V}{6k\Omega} = 0.5mA$$



$$i_{D1} = \frac{10V - 3V}{4k\Omega} = 1.75mA$$

$$i_{D2} = (i_{D1} + i_{D2}) - i_{D1} = 0.5 - 1.75 = -1.25mA$$


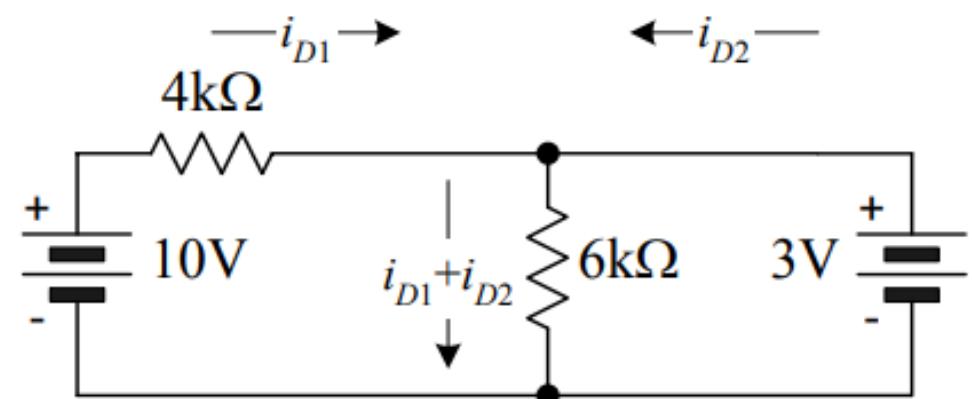


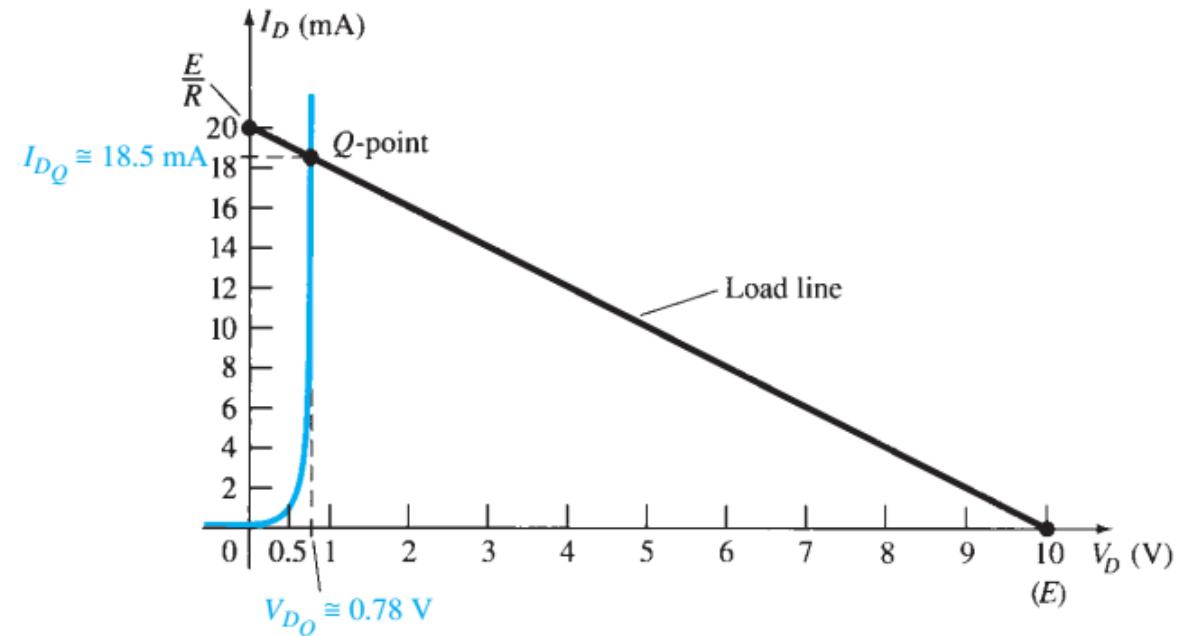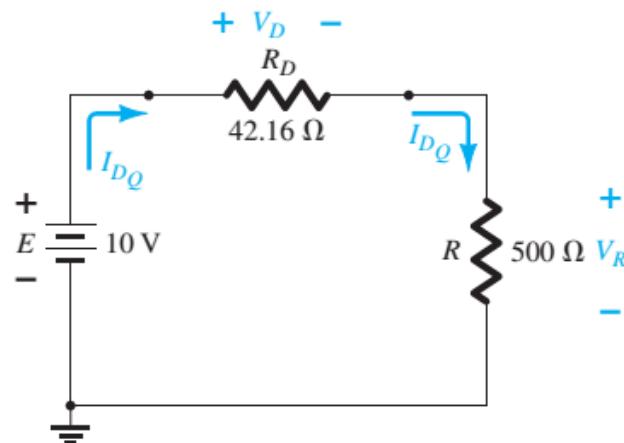Exercise 5

- Determine V_D , I_D and V_R based on the characteristic of the diode given in the following figure.



Solution (Ex. 5)

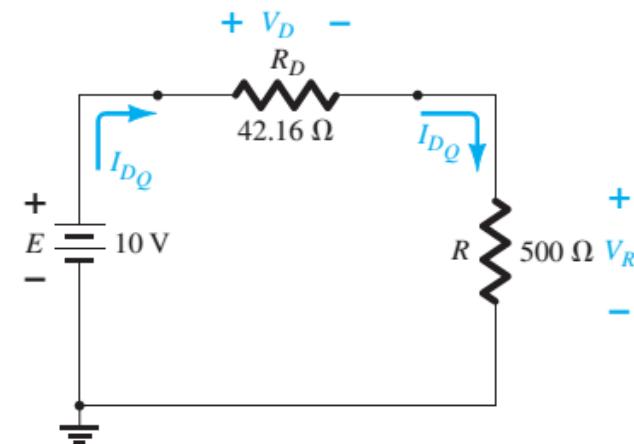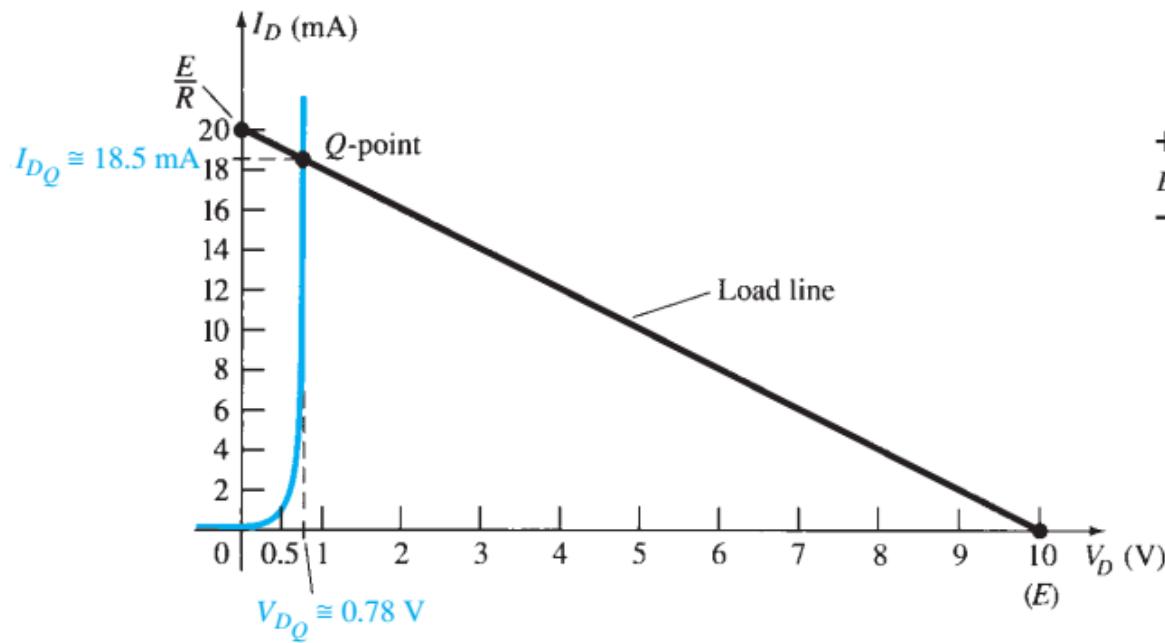


$$V_R = E - V_D = 10 \text{ V} - 0.78 \text{ V} = 9.22 \text{ V}$$



Exercise 6


- Given circuit
 - Reverse current $I_R = 1 \mu\text{A}$

- Determine V_F , I_F and V_R for three diode model
 - Ideal diode model
 - Practical diode model
 - Complete diode model

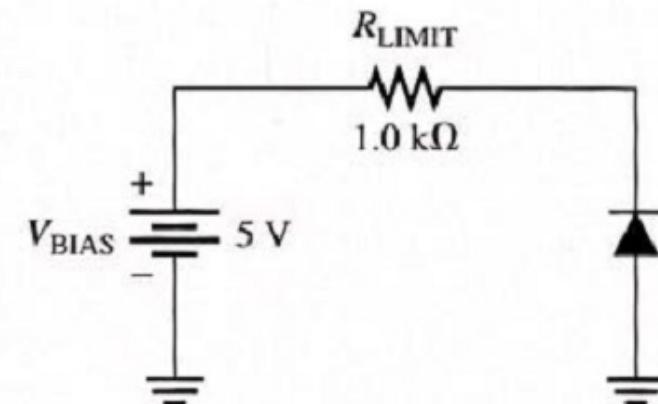


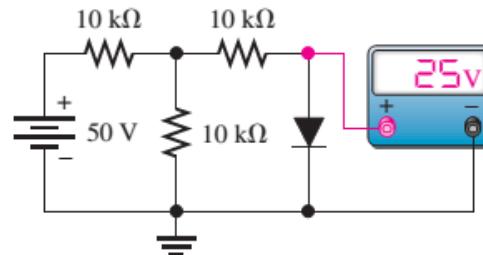Exercise 7


- Analyze and validate the value of the voltmeter in case of using ideal diode model ?




(a)

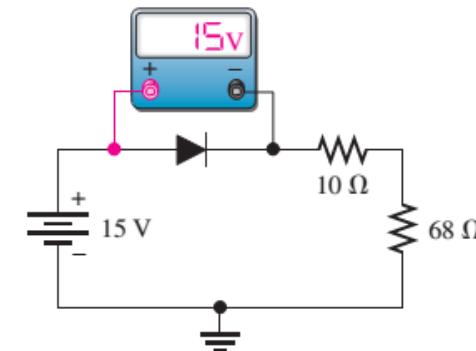

(b)

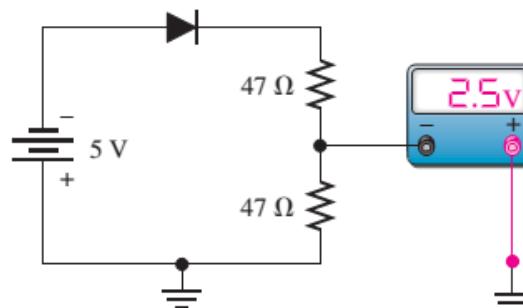

(c)

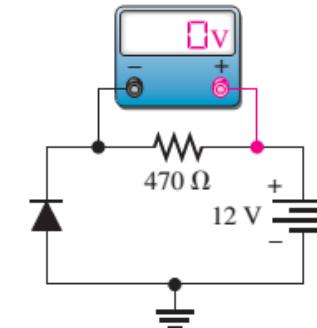

(d)